


* TWO PORT NETWORKS *

Introduction :-

Eg :- BJT, MOSFETS, opamps.

Two port \rightarrow Two pair of terminals

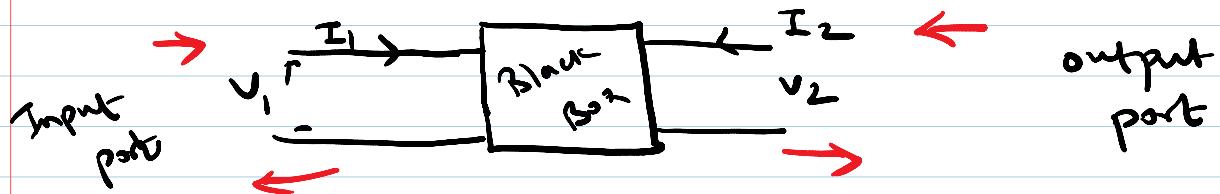Two port N/w \rightarrow is a electrical N/w with two pair of terminals to connect to external circuits.



Need:-

2 port N/w model \rightarrow ① Mathematical circuit analysis technique,

② isolate portions of larger circuits

Eg \rightarrow filters, transmission lines, transformers.

4 variables \rightarrow V_1, V_2, I_1, I_2 .

2 variables $\xrightarrow{\text{expressed}}$

$$4c_2 = \frac{n!}{v!(n-v)!} = \frac{6}{3!} = 6$$

2 variables

| Parameter | Express in terms of | Int terms of | Equation |
|-------------|---------------------|--------------|--|
| 1) Z | V_1, V_2 | I_1, I_2 | $V_1 = Z_{11}I_1 + Z_{12}I_2$ $V_2 = Z_{21}I_1 + Z_{22}I_2$ |
| 2) γ | I_1, I_2 | V_1, V_2 | |
| 3) ABCD | V_1, I_1 | V_2, I_2 | |

| | | | |
|----|----------------|--|--|
| 3) | ABCD | $\begin{vmatrix} v_1, i_1 \\ v_2, i_2 \end{vmatrix}$ | $\begin{vmatrix} v_2, i_2 \\ v_1, i_1 \end{vmatrix}$ |
| 4) | $A'B'C'D$ | $\begin{vmatrix} v_2, i_2 \\ v_1, i_1 \end{vmatrix}$ | v_1, i_1 |
| 5) | Hybrid | $\begin{vmatrix} v_1, i_2 \\ v_1, i_2 \end{vmatrix}$ | i_1, v_2 |
| 6) | Inverse hybrid | $\begin{vmatrix} i_1, v_2 \\ i_1, v_2 \end{vmatrix}$ | v_1, i_2 |

① Z-Parameters (open circuit impedance)

$$(v_1, v_2) = f(i_1, i_2)$$

$$\begin{aligned} v_1 &= z_{11} i_1 + z_{12} i_2 \quad |_{\substack{\text{zero} \\ \text{zero}}} \\ v_2 &= z_{21} i_1 + z_{22} i_2 \quad |_{\substack{\text{zero} \\ \text{zero}}} \\ v &= Z \frac{i}{I} \quad |_{\substack{\text{zero} \\ \text{zero}}} \end{aligned}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Case 1:- $i_2 = 0$ ($0 \cdot c$ o/p port)

$$z_{11} = \frac{v_1}{i_1} \Big|_{i_2=0}$$

z_{11} = $0 \cdot c$ input impedance or driving point impedance with $i_2 = 0$

$$z_{21} = \frac{v_2}{i_1} \Big|_{i_2=0}$$

z_{21} = $0 \cdot c$ forward transfer impedance

Case 2 :- $I_1 = 0$ (I_1 port is open circuit)


$$Z_{12} = \frac{V_1}{I_2} \quad | \quad I_1 = 0$$

$Z_{12} = 0\Omega$ reverse transfer impedance.


$$Z_{22} = \frac{V_2}{I_2} \quad | \quad I_1 = 0$$

Z_{22} = output impedance -

Equivalent circuit of 2 port $\text{n}\text{j}\omega$

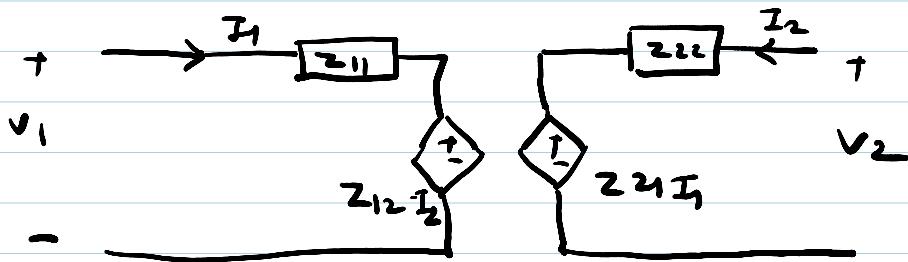

Ex. 1

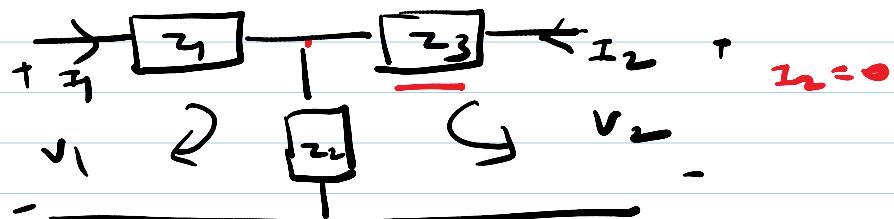

Z parameters?

\Rightarrow 1st method \rightarrow mesh analysis

2nd method \rightarrow 2 port $\text{n}\text{j}\omega$

$$I_2 = 0$$

$$V_1 = (Z_1 + Z_3) I_1 \quad \text{--- (1)}$$

$$Z_{11} = \frac{V_1}{I_1} \quad | \quad I_1 = 0 = \boxed{Z_1 + Z_3}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \boxed{Z_1 + Z_2}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$V_2 = Z_2 I_1 \quad (2)$$

$$\therefore \boxed{Z_{21} = Z_2}$$

$$I_1 = 0$$

$$V_2 = (Z_2 + Z_3) I_2 \rightarrow (3)$$

$$V_1 = Z_2 I_2 \rightarrow (4)$$

$$\boxed{Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = Z_2 Z_3}$$

$$\boxed{Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = Z_2}$$


Z - parameters are

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_1 + Z_2 & Z_2 \\ Z_2 & Z_2 + Z_3 \end{bmatrix}$$

Note:- Problems are based on R, L, C.

Transformed N/W \rightarrow R, L, $\frac{1}{C}$

Series - - -

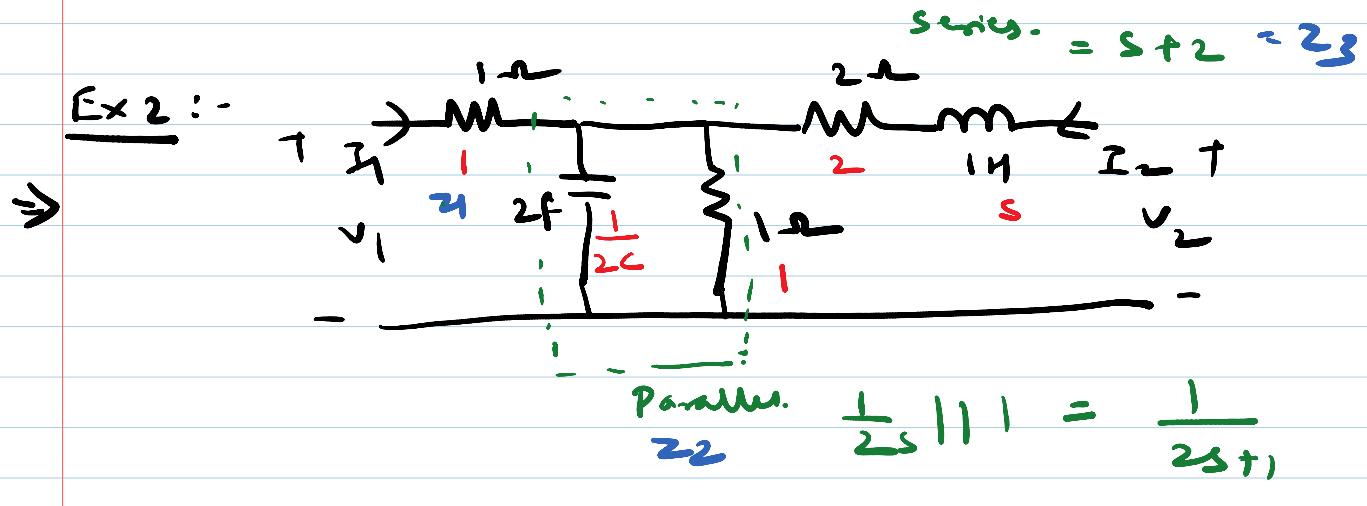

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_1 + Z_2 = 1 + \frac{1}{2s+1}$$

$$Z_{11} = \frac{2s+2}{2s+1}$$

$$Z_{12} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_2 = \frac{1}{2s+1} //$$

$$Z_{21} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_1 = \frac{1}{2s+1} //$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_3 + Z_4 = \frac{1}{2s+1} + s + 2$$

$$Z_2 = \frac{2s^2 + 5s + 3}{2s+1}$$

12/07/21
11:30 am


Condition of Reciprocity :-

- A π /w is said to be reciprocal if

ratio of excitation at one port to response at other port is same if excitation & response are interchanged.

Case 1 :-
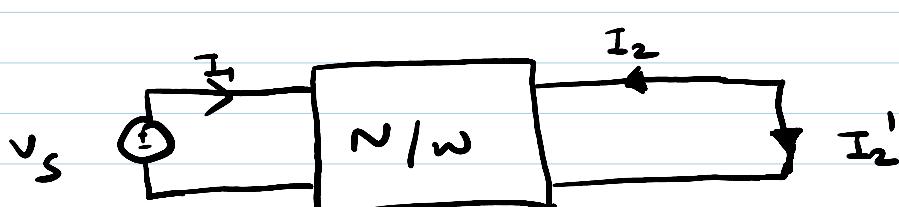
$$v_1 = v_s ; v_2 = 0 \quad I_2 = -I_2' \quad *$$



From Z parameter equations

$$\underline{v_s} = z_{11} \underline{I_1} - z_{12} \underline{I_2'} \quad *$$

$$0 = z_{21} \underline{I_1} - z_{22} \underline{I_2}'$$

$$I_1 = \frac{z_{22}}{z_{21}} I_2'$$

$$v_s = z_{11} \frac{z_{22}}{z_{21}} I_2' - z_{12} I_2'$$

$$\boxed{\frac{v_s}{I_2'} = \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{21}}}$$

Case 2 :- $v_2 = v_s ; v_1 = 0 \quad I_1 = -I_1'$



From Z parameter equations

$$0 = -z_{11} I_1' + z_{12} I_2$$

$$\underline{V_S} = -z_{21} \underline{I_1'} + z_{22} I_2$$

$$I_2 = \frac{z_{11}}{z_{12}} I_1'$$

$$\underline{V_S} = -z_{21} \underline{I_1'} + z_{22} \frac{z_{11}}{z_{12}} \underline{I_1'}$$

$$\frac{V_S}{I_1'} = \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{12}}$$

Networks to be reciprocal

$$\frac{V_S}{I_1'} = \frac{V_S}{I_2'}$$

$$z_{12} = z_{21}$$

Condition for Symmetry :-

The $\frac{V}{I}$ ratio at one port should be the same as $\frac{V}{I}$ ratio at other port with one

of the ports o.c.

Case 1:- $I_2 = 0$ (o/p port is o.c)

$$V_S = Z_{11} I_1$$

$$\boxed{\frac{V_S}{I_1} = Z_{11}}$$

case 2 :- $I_1 = 0$

$$V_S = Z_{22} I_2$$

$$\boxed{\frac{V_S}{I_2} = Z_{22}}$$

Z to be Symmetrical

$$\boxed{Z_{11} = Z_{22}}$$

Short Circuit Admittance Parameters (Y)

$$(I_1, I_2) = f(V_1, V_2)$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad V_2 = 0$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad V_1 = 0$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y] [V]$$

Case 1 :- $V_2 = 0$ (o/p port S.C)

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad \begin{array}{l} \text{S.C input admittance} \\ \text{or} \\ \text{driving pt} \end{array}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad \begin{array}{l} \text{S.C forward transfer} \\ \text{admittance} \end{array}$$


case 2 :- $V_1 = 0$ (i/p port S.C)

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad \begin{array}{l} \text{S.C reverse transfer} \\ \text{admittance} \end{array}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \quad \begin{array}{l} \text{S.C o/p admittance} \end{array}$$

The .. equivalent circuit of 2 port N/W in terms of

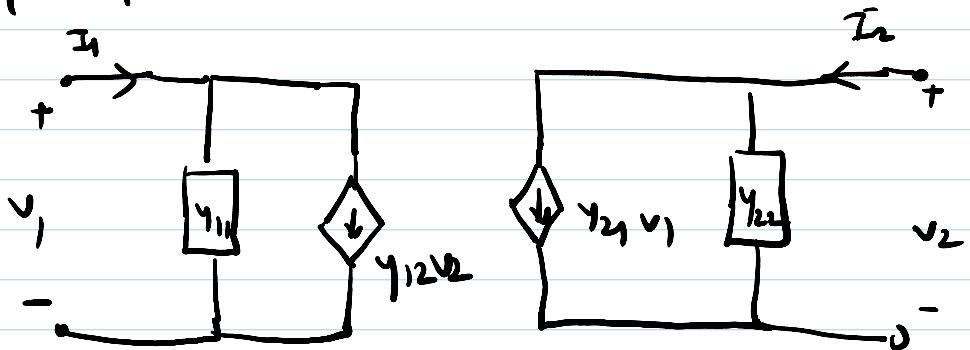The γ equivalent circuit of 2 port Nw in terms of parameter is



~~H.W~~

Condition of reciprocity

$$\frac{I_2'}{V_S} = \frac{I_1'}{V_S}$$


$$Y_{12} = Y_{21}$$

Condition of Symmetry

$$\frac{V_S}{I_1} = \frac{V_S}{I_2}$$

$$Y_{11} = Y_{22}$$

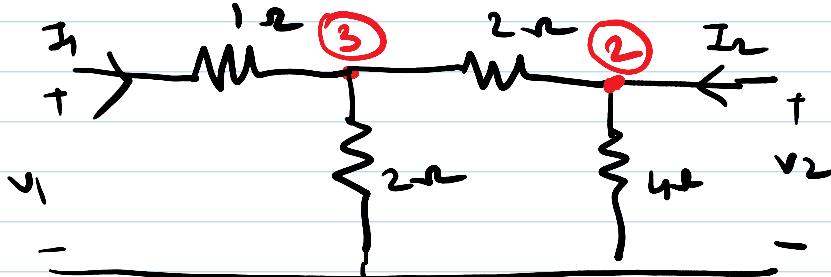- * Determine γ parameters & also findout whether the Nw is reciprocal & symmetrical



⇒ KCL at node 3 & 2

$$I_1 = \frac{v_3}{2} + \frac{v_3 - v_2}{2}$$

$$I_1 = \frac{\cancel{v_3}}{\gamma} - \frac{v_2}{2}$$

(1)

γ para?

$$I_2 = \frac{v_2}{4} + \frac{v_2 - v_3}{2}$$

$$\begin{aligned} I_1 &= v_1 \\ I_2 &= \gamma v_2 \end{aligned}$$

but

$$I_2 = \frac{3}{4}v_2 - \frac{\cancel{v_3}}{2}$$

(2)

$$I_1 = v_1 - \cancel{v_3}$$

(3)

Sub eqn (3) in (1)

$$v_1 - v_3 = v_3 - \frac{v_2}{2}$$

(4)

$$v_3 = \frac{v_1}{2} + \frac{v_2}{4}$$

Sub eqn (4) in (1) & (2)

$$I_1 = \underline{\frac{v_1}{2} + \frac{v_2}{4}} - \frac{-v_2}{2}$$

$$I_1 = \frac{v_1}{2} - \frac{v_2}{4} \rightarrow (5) \quad \checkmark$$

$I_1 = v_1$

$$\boxed{\gamma_{11} = \frac{1}{2} \quad \gamma_{12} = -\frac{1}{4}}$$

$$I_2 = \frac{3}{4}v_2 - \frac{1}{2} \left(\frac{v_1}{2} + \frac{v_2}{4} \right)$$

$$I_2 = \frac{3}{4}v_2 - \frac{1}{2}\left(\frac{v_1}{2} + \frac{v_2}{4}\right)$$


$$I_2 = -\frac{v_1}{4} + \frac{5}{8}v_2$$

$$Y_{11} = -\frac{1}{4} \quad Y_{22} = \frac{5}{8}$$


$$Y = \begin{bmatrix} \frac{1}{2}^+ & -\frac{1}{4}^- \\ -\frac{1}{4}^+ & \frac{5}{8}^* \end{bmatrix}$$

$Y_{11} \neq Y_{22}$, Not symmetrical

$Y_{12} = Y_{21}$, N/w is reciprocal

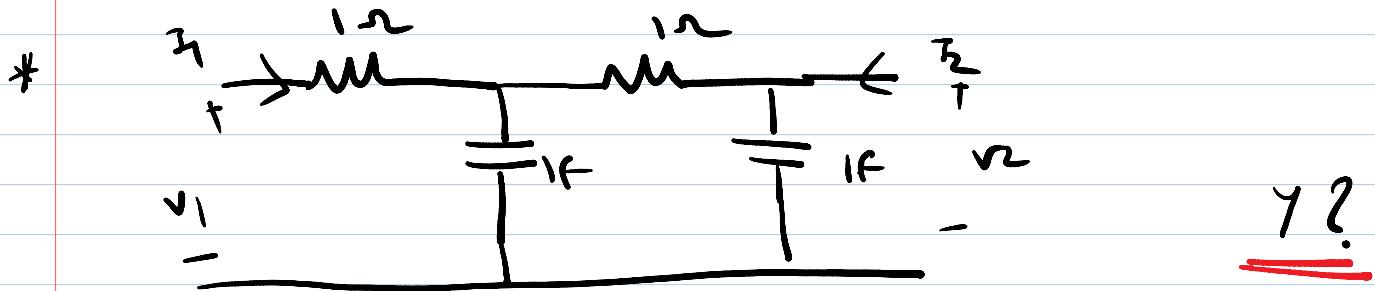

⇒ Transform the N/w

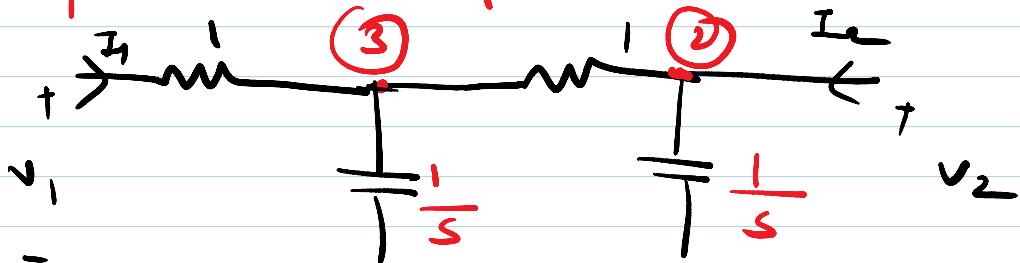

$$= \frac{1}{T\frac{1}{s} + T\frac{1}{s} - v_2}$$

Apply KCL at node (3) 4 (2)

$$I_1 = sV_3 + V_3 - V_2$$

$$I_1 = (s+1)V_3 - V_2 \quad -\textcircled{1}$$

$$I_2 = sV_2 + V_2 - V_3$$

$$= (s+1)V_2 - V_3 \quad -\textcircled{2}$$

$$I_1 = V_1 - V_3 \quad -\textcircled{3}$$

Sub. I_1 in eqn $\textcircled{1}$

$$V_1 - V_3 = (s+1)V_3 - V_2$$

$$\therefore V_3 = \frac{V_1}{s+2} + \frac{V_2}{s+2} \quad \textcircled{4}$$

Sub $\textcircled{4}$ in $\textcircled{1} \textcircled{2}$

$$Y = \begin{bmatrix} \frac{s+1}{s+2} & -\frac{1}{s+2} \\ -\frac{1}{s+2} & \frac{s^2+3s+1}{s+2} \end{bmatrix}$$

13/07/2021

Tuesday, July 13, 2021
2:11 PM

Transmission parameters (ABCD) / chain

$$* \quad v_1, v_2 = f(I_1, I_2) \rightarrow Z \rightarrow 0 \cdot C \rightarrow I_2 = 0$$

$$* \quad I_1, I_2 = f(v_1, v_2) \rightarrow Y \rightarrow S \cdot C \rightarrow v_2 = 0$$

$$* \quad v_1, I_1 = f(v_2, I_2)$$

$$v_1 = Av_2 - BI_2 \quad I_2 = 0 \quad v_2 = 0$$

$$I_1 = Cv_2 - DI_2$$

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$

transmission matrix

$v_2 = 0$
 $I_2 = 0$

Case 1 :- When o/p port is $0 \cdot C$ $I_2 = 0$

$$A = \frac{v_1}{v_2} \Big|_{I_2=0} \quad \text{reverse ref. gain}$$


$$C = \frac{I_1}{v_2} \Big|_{I_2=0} \quad \text{transfer admittance}$$

Case 2 :- When o/p port is $S \cdot C$ ie $v_2 = 0$

$$B = -\frac{v_1}{I_2} \Big|_{v_2=0} \quad \text{transfer impedance}$$

$$D = - \frac{I_1}{I_2} \Big|_{V_2=0} \quad \text{reverse current gain}$$

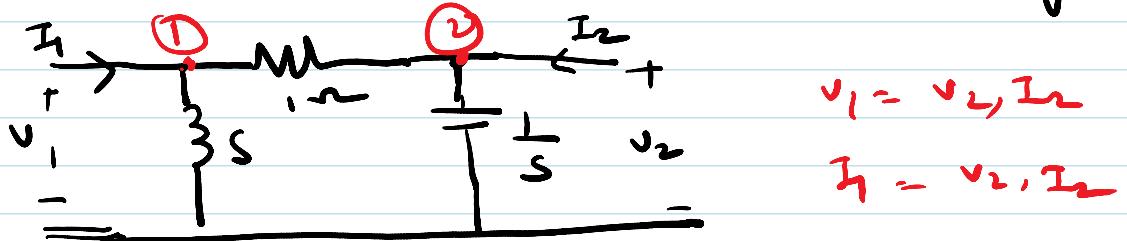* Determine ABCD parameters for the n/w given



$$V_1 = V_2, I_2$$

$$I_1 = V_2, I_2$$

⇒ Apply KCL at node ① & ②

$$I_1 = \frac{V_1}{s} + V_1 - V_2 \quad V_1 = V_2, I_2$$

$$I_1 = \left(\frac{s+1}{s} \right) V_1 - V_2 \rightarrow ① \quad I_1 = V_2, I_2$$

$$I_2 = sV_2 + V_2 - V_1$$

$$I_2 = (s+1)V_2 - V_1 \rightarrow ②$$

Rearrange


$$V_1 = (s+1)V_2 - I_2 \rightarrow ③$$

Sub. eqn ③ in eqn ①

$$I_1 = \frac{s+1}{s} \left[(s+1)V_2 - I_2 \right] - V_2$$

$$I_1 = \left[\frac{(s+1)^2}{s} - 1 \right] V_2 - \frac{s+1}{s} I_2 \rightarrow ④$$
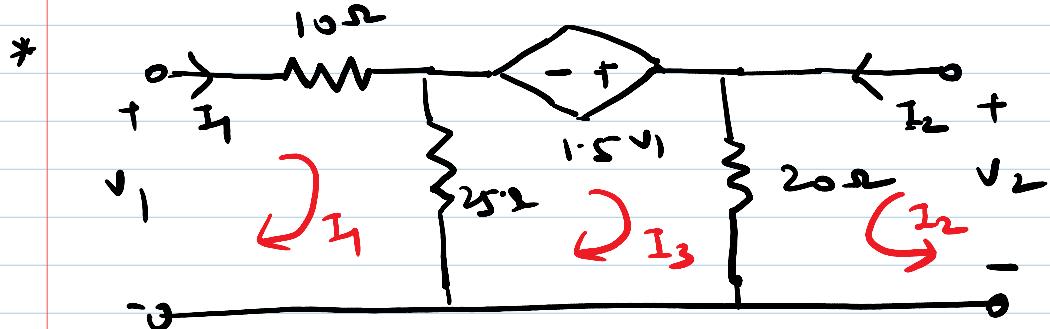
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} s+1 & +1 \\ \frac{s^2+s+1}{s} & \frac{+s+1}{s} \end{bmatrix}$$



\Rightarrow Applying KVL 1, 2, & 3.

$$v_1 = 35I_1 - 25I_3 \quad \textcircled{1}$$

$$v_2 = 20I_2 + 20I_3 \quad \textcircled{2}$$

$$-25(I_3 - I_1) + 1.5v_1 - 20(I_2 + I_3) = 0$$

$$\cancel{-25I_3} + 25I_1 + 1.5(35I_1 - \cancel{25I_3}) - 20I_2 - \cancel{20I_3} = 0$$

$$-25I_3 + 25I_1 + 52.5I_1 - 37.5I_3 - 20I_2 - 20I_3 = 0$$

$$82.5I_3 = 77.5I_1 - 20I_2$$

$$I_3 = 0.94I_1 - 0.24I_2 \quad \textcircled{3}$$

Sub eqn 3 \rightarrow eqn 1

$$v_1 = 35I_1 - 25(0.94I_1 - 0.24I_2)$$

$$v_1 = 11.5I_1 + 6I_2 \rightarrow \textcircled{4}$$

$$V_1 = 11.5 I_1 + 6 I_2 \rightarrow \textcircled{4}$$

2

Sub eqn 3 \rightarrow eqn ②

$$V_2 = 20 I_2 + 20(0.94 I_1 - 0.24 I_2) \quad \textcircled{1}$$

$$V_2 = 18.8 I_1 + 15.2 I_2 \rightarrow \textcircled{5}$$

Rearranging \rightarrow eqn ③

$$I_1 = 0.053 V_2 - 0.81 I_2 \quad \checkmark_{C,D}$$

From eqn ④

$$V_1 = 11.5 \left(\frac{0.053 V_2 - 0.81 I_2}{I_1} \right) + 6 I_2 \rightarrow \textcircled{6}$$


$$V_1 = f(V_2, I_2) \quad \checkmark \quad A, B.$$

$$V_1 = 0.61 V_2 - 3.3 I_2 \quad \checkmark \quad A, B$$

$$\boxed{\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.61 & 3.32 \\ 0.053 & 0.81 \end{bmatrix}}$$

* Condition for Reciprocity

Case 1 :-

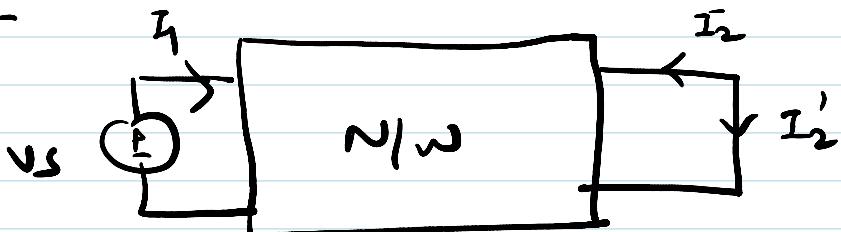

$$V_1 = V_S$$

$$V_2 = 0$$


$$I_2' = -I_2$$

Sub. in Standard ABCD eqn.

$$V_S = B I_2'$$

$$\frac{v_s}{I_2'} = B \quad (1)$$

Case 2 i -

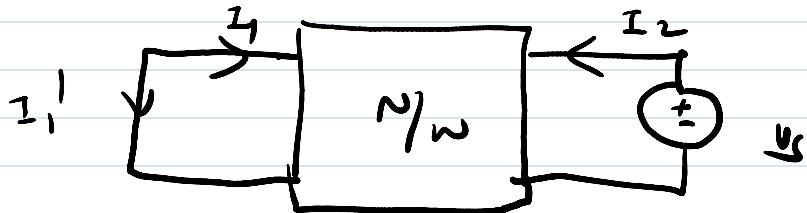

$$v_2 = v_s$$

$$v_1 = 0$$

$$I_1' = -I_2$$

Sub in standard ABCD eqn.

$$0 = A v_s - B I_2$$

$$-I_1' = C v_s - D I_2$$

$$I_2 = \frac{A}{B} v_s$$

$$-I_1' = C v_s - \frac{AD}{B} v_s$$

$$\frac{v_s}{I_1'} = \frac{B}{AD - BC} \rightarrow (2)$$

\sim/ω to be real, pos,

$$\frac{v_s}{I_1'} = \frac{v_s}{I_2'}$$

$$\frac{B}{AD - BC} = B$$

$$AD - BC = 1$$

*

Condition for Symmetry :-

Condition for Symmetry :-

Case 1 :- $I_2 = 0$

$$V_S = A V_2$$

$$I_1 = C V_2$$

$$\frac{V_S}{I_1} = \frac{A}{C} \quad \textcircled{1}$$

Case 2 :- $I_1 = 0$

$$C V_S = D I_2$$

$$\therefore \frac{V_S}{I_2} = \frac{D}{C} \quad \textcircled{2}$$

N/w to be symmetrical

$$\frac{V_S}{I_1} = \frac{V_S}{I_2}$$

$$\boxed{A = D}$$

Hybrid Parameters (h parameters)

$$(V_1, V_2) = f(I_1, I_2) \rightarrow z$$

$$(I_1, I_2) = f(V_1, V_2) \rightarrow y$$

$$(V_1, I_2) = f(V_2, -I_2) \rightarrow ABCD$$

Hybrid parameters

$$(V_1, I_2) = f(I_1, V_2) \rightarrow h$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \quad \begin{array}{l} \rightarrow \text{zero} \\ \rightarrow \text{zero} \end{array}$$

$$h_{11}=? \quad h_{12}=? \quad \dots$$

Case 1 :- $V_2 = 0$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad \text{s.c } 1/p \text{ impedance}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \quad \text{s.c forward current gain}$$

Case 2 :- $I_1 = 0$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad \text{o.c reverse v.o. gain}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \text{O.C o/p admittance}$$

Equivalent circuit :-



Condition of reciprocity :-

$$\frac{V_s}{I_2'} = \frac{V_s}{I_1'}$$

$$h_{21} = -h_{12}$$

Condition for symmetry :-

$$h_{11}h_{22} - h_{12}h_{21} = 1$$

| Parameter | Condition for reciprocity | Condition for symmetry |
|-----------|-----------------------------|-----------------------------|
| Z | $Z_{12} = Z_{21}$ | $Z_{11} = Z_{22}$ |
| γ | $\gamma_{12} = \gamma_{21}$ | $\gamma_{11} = \gamma_{22}$ |
| $ABCD$ | $AD - BC = 1$ | $A = D$ |

| | | |
|-----|--------------------|-----------------------------------|
| h | $h_{12} = -h_{21}$ | $h_{11}h_{22} - h_{21}h_{12} = 1$ |
|-----|--------------------|-----------------------------------|

* Compute h parameters if

(a) $V_1 = 25V$, $I_1 = 1A$, $I_2 = 2A \rightarrow$ o/p port s.c

(b) $V_1 = 10V$ $V_2 = 50V$ $I_2 = 2A \rightarrow$ o/p port o.c

$$\Rightarrow V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

(a) o/p port is s.c $V_2 = 0$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \underline{\underline{25 \Omega}}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \underline{\underline{2}}$$


(b) o/p port is o.c $I_1 = 0$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{10}{50} = \underline{\underline{0.2}}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{2}{50} = \underline{\underline{0.04V}} =$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 25 & 0.2 \\ 2 & 0.04 \end{bmatrix}$$

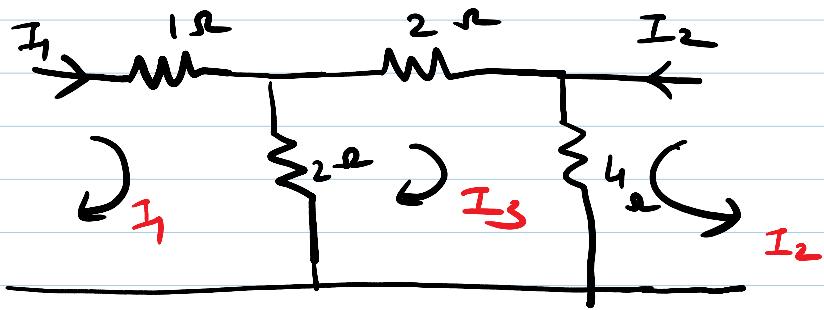- * For the given \mathbf{N}/\mathbf{W} determine whether \mathbf{N}/\mathbf{W} is reciprocal.



$\Rightarrow \mathbf{N}/\mathbf{W}$ to be reciprocal

$$h_{12} = -h_{21}$$

$$V_1 = f(I_1, V_2)$$

$$I_2 = f(I_1, V_2)$$

Apply KVL to mesh 1, 2 & 3

$$V_1 = 3I_1 - 2I_3 \quad \text{---} \quad (1)$$

$$V_2 = 4I_2 + 4I_3 \quad \text{---} \quad (2)$$

$$-2(I_3 - I_1) - 2I_3 - 4(I_3 + I_2) = 0$$

$$-8I_3 + 2I_1 - 4I_2 = 0$$

$$I_3 = \frac{I_1}{4} - \frac{I_2}{2} \quad \text{---} \quad (3)$$

Sub eqn 3 in (1) & (2)

$$V_1 = 3I_1 - 2\left(\frac{I_1}{4} - \frac{I_2}{2}\right)$$

$$V_1 = \frac{5}{2}I_1 + I_2 \quad \text{---} \quad (4)$$

$$V_2 = 4I_2 + 4\left(\frac{I_1}{4} - \frac{I_2}{2}\right)$$

$$v_2 = I_1 + 2I_2 \rightarrow (5)$$

rearrange can
in (5)

$$I_2 = -\frac{I_1}{2} + \frac{1}{2}v_2 \rightarrow (6)$$

h_{11} h_{22}

Sub. I_2 in eqn (4)

$$v_1 = \sum_{j=1}^2 I_j - \frac{I_1}{2} + \frac{1}{2}v_2$$

$$v_1 = 2I_1 + \frac{1}{2}v_2 \rightarrow (6)$$



h_{11} h_{12}


$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2 & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

Yes, N/W is reciprocal

$$h_{12} = -h_{21}$$

Answer.

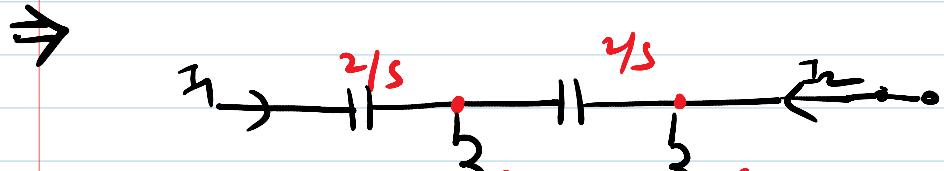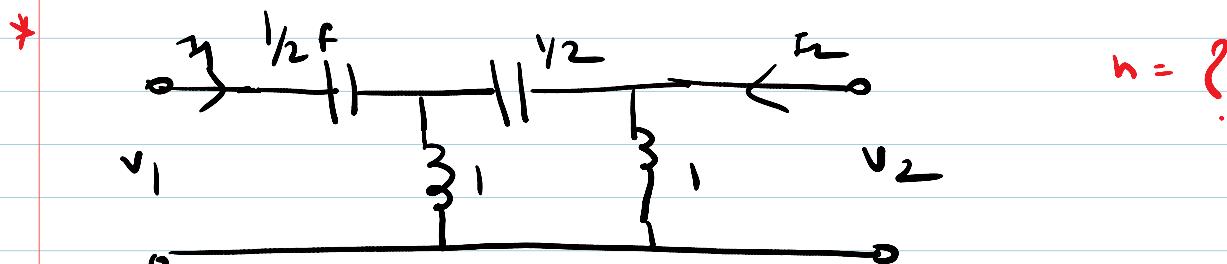

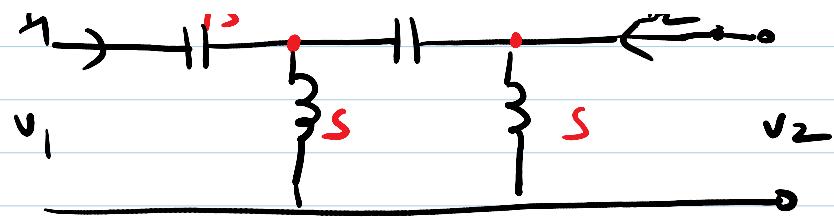

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{4(s^2 + 1)}{s(s^2 + 2)} & \frac{s^2}{s^2 + 2} \\ -\frac{s^2}{s^2 + 2} & \frac{2(s^2 + 1)}{s(s^2 + 2)} \end{bmatrix}$$

14/07/21 | 2:15 PM

Wednesday, July 14, 2021
1:06 PM

Interrelationship between the parameters

* Z parameters in terms of other parameters

i) Z parameters in terms of γ Parameters

$$\Rightarrow \gamma \text{ parameter } (I_1, I_2) = f(v_1, v_2)$$

$$I_1 = \gamma_{11} v_1 + \gamma_{12} v_2$$

$$I_2 = \gamma_{21} v_1 + \gamma_{22} v_2$$

$$Z = ? \quad (v_1, v_2) = f(I_1, I_2)$$

$$v_1 = ?$$

$$v_2 = ?$$

Cramer's rule

$$v_1 = \frac{\begin{vmatrix} I_1 & \gamma_{12} \\ I_2 & \gamma_{22} \end{vmatrix}}{\begin{vmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{vmatrix}} = \frac{\gamma_{22} I_1 - \gamma_{12} I_2}{\gamma_{11} \gamma_{22} - \gamma_{12} \gamma_{21}}$$

$$\underline{v_1} = \frac{\gamma_{22}}{\Delta \gamma} \underline{I_1} - \frac{\gamma_{12}}{\Delta \gamma} \underline{I_2}$$

$$\Delta \gamma = \gamma_{11} \gamma_{22} - \gamma_{12} \gamma_{21}$$

$$Z_{11} = \frac{\gamma_{22}}{\Delta \gamma} \quad Z_{12} = \frac{\gamma_{12}}{\Delta \gamma}$$

$$v_2 = \frac{\begin{vmatrix} y_{11} & I_1 \\ y_{21} & I_2 \end{vmatrix}}{\begin{vmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{vmatrix}} = \frac{y_{11} I_2 - y_{21} I_1}{\Delta y} = \frac{y_{11} I_2 - \frac{y_{21}}{\Delta y} I_1}{\Delta y}$$

$$v_2 = -\frac{y_{21}}{\Delta y} I_1 + \frac{y_{11}}{\Delta y} I_2$$

$\underbrace{z_{21}}_{z_{22}}$

$$z_{21} = -\frac{y_{21}}{\Delta y} \quad z_{22} = \frac{y_{11}}{\Delta y}$$

* Z Parameters in terms of ABCD parameters

$$\Rightarrow z = l.$$

ABCD parameters

$$\begin{aligned} v_1 &= Av_2 - Bi_2 & (1) \\ i_1 &= Ci_2 - Di_2 & (2) \end{aligned} \quad \left. \begin{array}{l} z \\ v_1 = i_1 i_2 \\ v_2 = i_1 i_2 \end{array} \right\}$$

Rewrite the 2nd eqn

$$v_2 = \frac{i_1}{c} + \frac{d}{c} i_2 \quad (3)$$

$\underbrace{z_{21}}_{z_{22}}$

$$Z_{21} = \frac{1}{C}$$

$$Z_{22} = \frac{D}{C}$$

Sub eqn ③ in eqn ①

$$v_1 = I_1, I_2$$



$$v_1 = A \left[\frac{1}{C} I_1 + \frac{D}{C} I_2 \right] - B I_2$$

$$v_1 = \frac{A}{C} I_1 - \frac{AD - BC}{C} I_2$$

Z_{11} Z_{12}

$$Z_{11} = \frac{A}{C} \quad Z_{12} = \frac{AD - BC}{C}$$

3) Z-parameters in terms of h parameters

$$Z = ?$$

$$v_1 = I_1, I_2$$



h parameters

$$v_2 = I_1, I_2$$

$$v_1 = h_{11} I_1 + h_{12} v_2 \quad ①$$

$$I_2 = h_{21} I_1 + h_{22} v_2 \quad ②$$

Rewrite the 2nd eqn

$$v_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \rightarrow ③$$

$$z_{21} = -\frac{h_{21}}{h_{22}} \quad z_{22} = \frac{1}{h_{22}}$$

Sub eqn ③ in eqn ①

$$v_1 = h_{11} I_1 + h_{12} \left[\frac{-h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right]$$

$$v_1 = h_{11} I_1 - \frac{h_{12} h_{21}}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$v_1 = \left(\frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right) I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$h_{11} h_{22} - h_{12} h_{21} = \Delta h$$

$$v_1 = \frac{\Delta h}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$z_{11} = \frac{\Delta h}{h_{22}} \quad z_{12} = \frac{h_{12}}{h_{22}}$$

* → γ parameter → $\begin{matrix} z \\ \text{eqn} \end{matrix}$ Cramers rule
 $A B C D \rightarrow$ Rewrite 1st eqn *
 Sub ③ in ②
 $h \rightarrow$ Rewrite 1st eqn *
 Sub ③ in ②

* $\text{ABCD} \rightarrow Z \rightarrow$ Rewrite 2nd eqn \rightarrow Sub 1st eqn

$$Y \rightarrow \quad , \quad " \quad "$$

$$h \rightarrow \quad " \quad , \quad \rightarrow \quad "$$

* $h \text{ parameters} \rightarrow Z \rightarrow$ Rewrite 2nd eqn \rightarrow sub



$Y \rightarrow$ Rewrite 1st eqn \rightarrow sub *

$\text{ABCD} \rightarrow$ Rewrite 2nd eqn \rightarrow sub

$$\begin{array}{c|cc|c} z_{11} & z_{12} & \frac{y_{22}}{\Delta y} - \frac{y_{12}}{\Delta y} \\ \hline z_2 & z_{22} & \frac{-y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{array}$$

$$\begin{array}{cc} y_{11} & y_{12} \\ y_{21} & y_{22} \end{array}$$

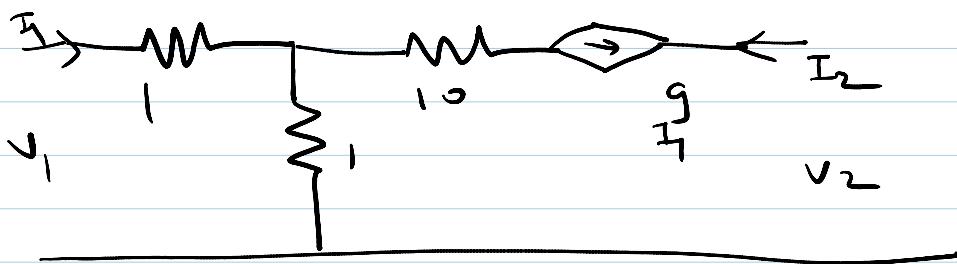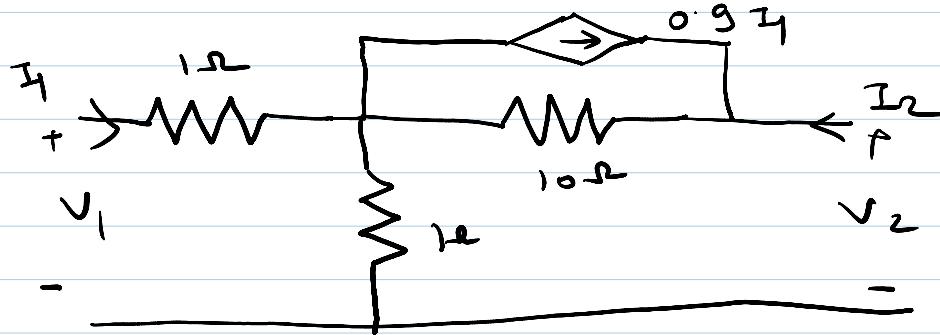* Find Z parameters & then find γ & h parameters



$$v_1 = \underline{2\gamma} + \underline{I_2} - \textcircled{1}$$

$$v_2 = \underline{10\gamma} + \underline{11I_2} \rightarrow \textcircled{2}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} 2 & 1 \\ 10 & 11 \end{bmatrix}$$

$$\Delta z = 12$$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{11}{12} v$$

$$y_{12} = \frac{z_{12}}{\Delta z} = \frac{1}{12} v$$

$$y_{21} = -\frac{z_{21}}{\Delta z} = -\frac{5}{6} v$$

$$y_{22} = \frac{z_{11}}{\Delta z} = \frac{1}{6} v$$

$$\begin{bmatrix} \frac{11}{12} & \frac{1}{12} \\ -\frac{5}{6} & \frac{1}{6} \end{bmatrix}$$


$$h_{11} = \frac{\Delta z}{z_{22}} = \frac{12}{11} v$$


$$h_{12} = \frac{z_{12}}{z_{22}} = \frac{1}{11}$$

$$h_{21} = -\frac{z_{21}}{z_{22}} = -\frac{10}{11}$$

$$\begin{bmatrix} \frac{12}{11} & \frac{1}{11} \\ -\frac{10}{11} & \frac{1}{11} \end{bmatrix}$$
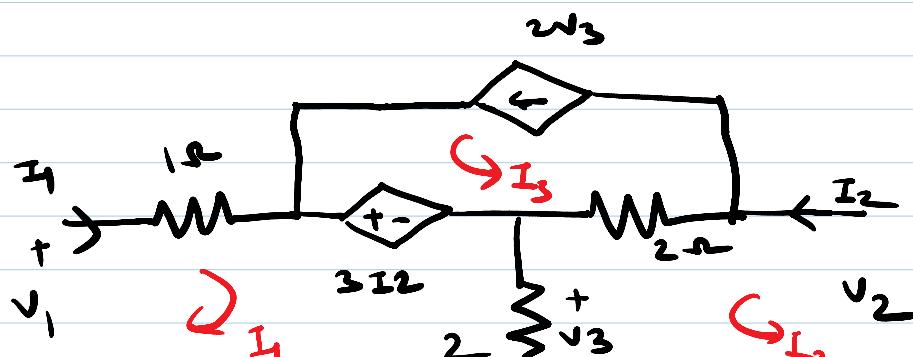
$$h_{22} = \frac{1}{z_{22}} = \frac{1}{11} v$$



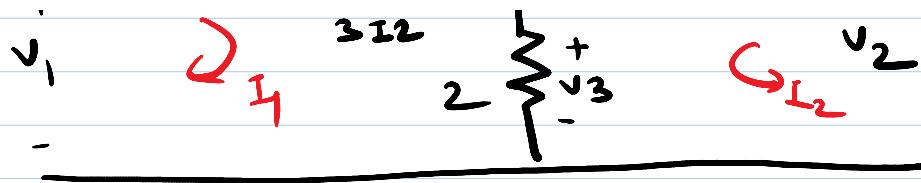


$$Z = \begin{bmatrix} 3 & 5 \\ -6 & -4 \end{bmatrix}$$

Interconnection of two port networks

- Cascade
- Parallel
- Series
- Series-parallel
- parallel-series

* Cascade Connection :-

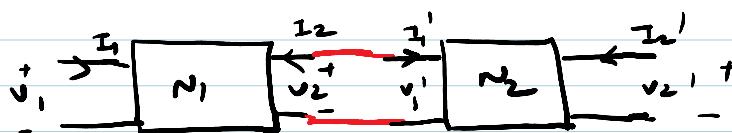

$$I_1' = -I_2$$

Let A_1, B_1, C, D_1 be transmission parameters of the network N_1 ,

Let $A_2, B_2, C_2 \& D_2$ " "

N_1 ,

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C & D_1 \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$

N_2 ,

$$\begin{bmatrix} v_1' \\ -I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_2' \\ -I_2' \end{bmatrix}$$

$$v_1' = v_2 \quad \text{and} \quad I_1' = -I_2$$


$$\begin{bmatrix} v_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_2' \\ -I_2' \end{bmatrix}$$

Combine.

$$\begin{bmatrix} v_1 \\ -I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_2' \\ -I_2' \end{bmatrix}$$

$$[A \ B] = [A_1 \ B_1] [A_2 \ B_2]$$

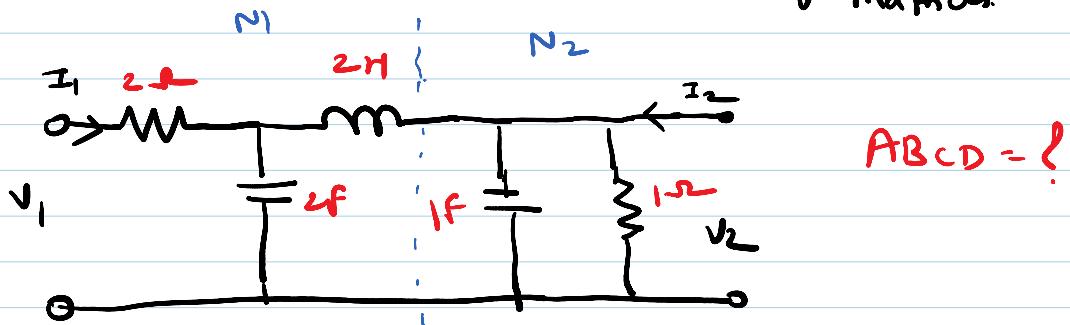
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \underbrace{\begin{bmatrix} A & B_1 \\ C & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}}_{\text{product of individual } AB \text{ and } CD \text{ matrices.}}$$



→ Cascade connection of two $N|N$ $N_1, 4N$,

new
Let N_1 Network

(Transformed $N|N$)

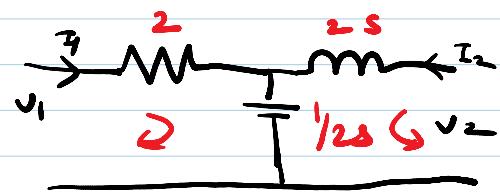

Apply KVL to mesh ① & ②

$$v_1 = \left(2 + \frac{1}{2s} \right) i_1 + \frac{1}{2s} i_2 \quad ①$$

$$v_2 = \frac{1}{2s} i_1 + \left(2s + \frac{1}{2s} \right) i_2 \quad ②$$

$$ABCD \rightarrow (v_1, i_1) \rightarrow f(v_2, -i_2)$$

$$\begin{aligned} v_1 &= v_2, -i_2 \\ i_1 &= v_2, -i_2 \end{aligned}$$

Rearrange eqn ②

$$i_1 = \frac{2s v_2}{2} - \frac{(4s^2 + 1)}{2} i_2 \rightarrow ③$$

Subs. eqn ③ in eqn ①

$$v_1 = \left(2 + \frac{1}{2s} \right) \left[2s v_2 - (4s^2 + 1) i_2 \right] + \frac{1}{2s} i_2$$

$$v_1 = \underbrace{(4s + 1)}_{A} v_2 - \underbrace{(8s^2 + 2s + 2)}_{B} i_2 \rightarrow ④$$

$$1 - \frac{14s+1}{s} = (s+2) \frac{A}{B}$$

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} = \begin{bmatrix} 4s+1 & 8s^2+2s+2 \\ 2s & 4s^2+1 \end{bmatrix}$$

Let Network $N_2 \rightarrow A_2 B_2 C_2 D_2$



Apply KVL to mesh ① & ②

$$v_1' = \frac{1}{s+1} i_1' + \frac{1}{s+1} I_2' \quad ①$$

$$v_2' = \frac{1}{s+1} i_1' + \frac{1}{s+1} I_2' \quad ②$$

$$i_1' = (s+1)v_2' - I_2' \quad -③$$

$$v_1' = v_2' \rightarrow ④$$

$$\begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ s+1 & 1 \end{bmatrix}$$


Overall ABCD

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 4s+1 & 8s^2+2s+2 \\ 2s & 4s^2+1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ s+1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \boxed{\quad}$$

$$\left[\begin{smallmatrix} \text{C} & \text{D} \end{smallmatrix} \right] - \left[\begin{smallmatrix} \text{L} \end{smallmatrix} \right]$$

Parallel connection:-

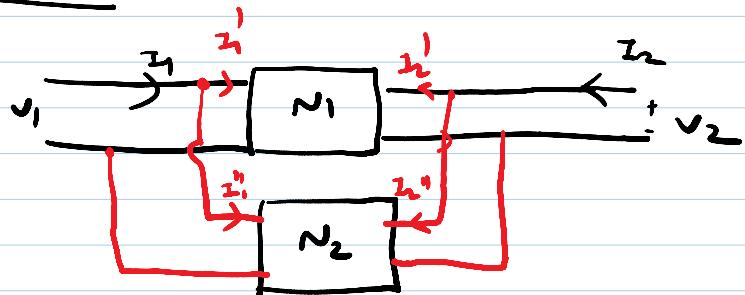

Y parameters -

$$N_1 \rightarrow Y_{11}', Y_{12}', Y_{21}', Y_{22}'$$

$$N_2 \rightarrow Y_{11}'', Y_{12}'', Y_{21}'', Y_{22}''$$


$$N_1 \rightarrow \begin{bmatrix} I_1' \\ I_2' \end{bmatrix} = \begin{bmatrix} Y_{11}' & Y_{12}' \\ Y_{21}' & Y_{22}' \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$N_2 \rightarrow \begin{bmatrix} I_1'' \\ I_2'' \end{bmatrix} = \begin{bmatrix} Y_{11}'' & Y_{12}'' \\ Y_{21}'' & Y_{22}'' \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$I_1 = I_1' + I_1'' \quad \Delta \quad I_2 = I_2' + I_2''$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11}' + Y_{11}'' & Y_{12}' + Y_{12}'' \\ Y_{21}' + Y_{21}'' & Y_{22}' + Y_{22}'' \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$
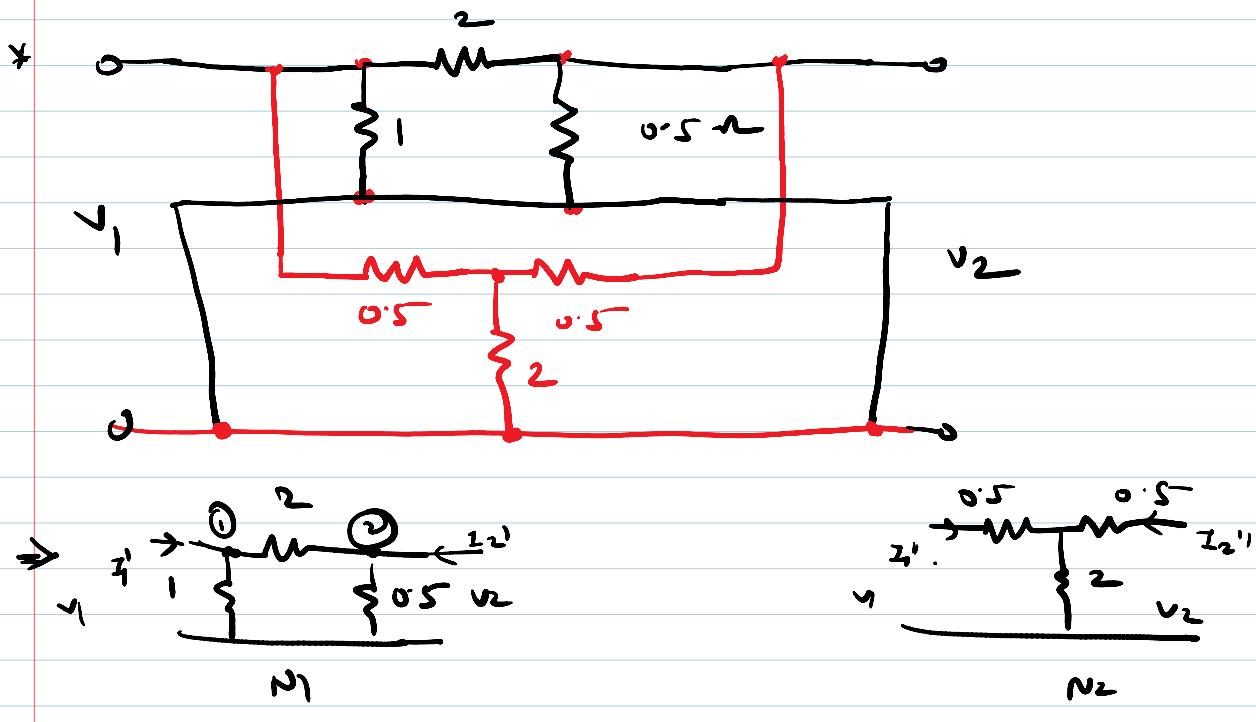
$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_1' + Y_{11}'' & Y_{12}' + Y_{12}'' \\ Y_{21}' + Y_{21}'' & Y_{22}' + Y_{22}'' \end{bmatrix}$$



Applying KCL

$$i_1' = \frac{3}{2}v_1 - \frac{1}{2}v_2$$

$$i_2' = \frac{v_2}{0.5} + \frac{v_2 - v_1}{2}$$

$$i_1'' = -\frac{1}{2}v_1 + \frac{5}{2}v_2$$

$$[Y] = \begin{bmatrix} 3/2 & v_2 \\ -1/2 & 5/2 \end{bmatrix}$$


$$[Y] = \begin{bmatrix} 10/9 & -8/9 \\ -8/9 & 10/9 \end{bmatrix}$$

$$[Y] = \begin{bmatrix} 3/2 + 10/9 & v_2 - 8/9 \\ -v_2 - 8/9 & 5/2 - 10/9 \end{bmatrix}$$

$$[Y] = \begin{bmatrix} 47/18 & -25/18 \\ -25/18 & -5/18 \end{bmatrix}$$

16/07/21

Series Connection :-

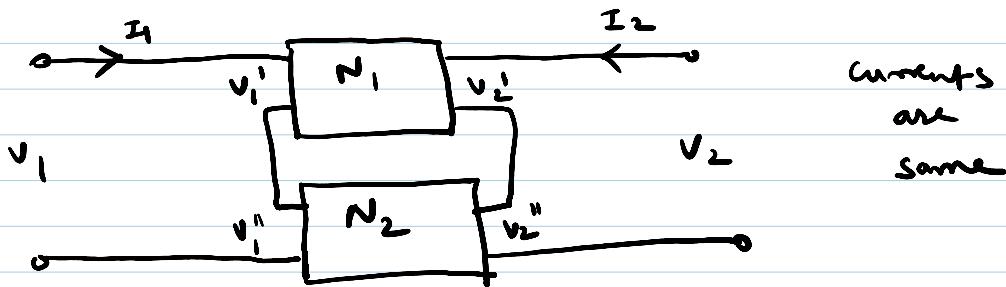

$$\text{Let } z_{11}', z_{12}', z_{21}' \text{ & } z_{22}' \rightarrow N_1 \text{ N/w}$$

$$\text{and } z_{11}'', z_{12}'', z_{21}'' \text{ & } z_{22}'' \rightarrow N_2 \text{ N/w}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11}' & z_{12}' \\ z_{21}' & z_{22}' \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


$$\begin{bmatrix} v_1'' \\ v_2'' \end{bmatrix} = \begin{bmatrix} z_{11}'' & z_{12}'' \\ z_{21}'' & z_{22}'' \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


$$v_1 = v_1' + v_1'' \quad v_2 = v_2' + v_2''$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11}' + z_{11}'' & z_{12}' + z_{12}'' \\ z_{21}' + z_{21}'' & z_{22}' + z_{22}'' \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\underbrace{\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}}_{\text{Sum of Z matrices.}}$$

Series - Parallel Connection :-

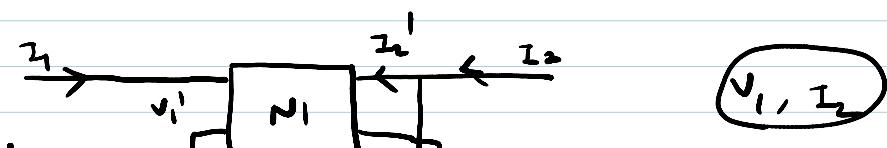

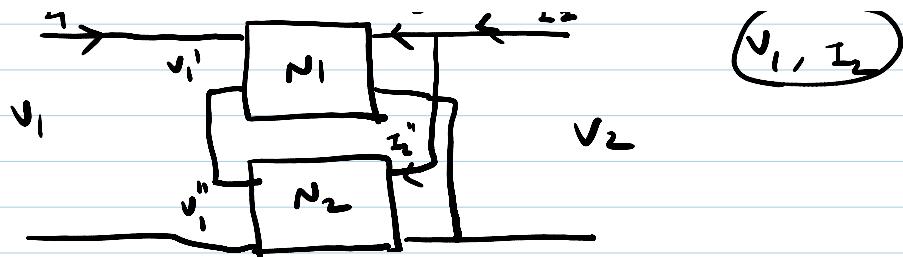

h -parameters $\rightarrow h_{11}', h_{12}', h_{21}' \rightarrow N_1$
 $h_{11}'', h_{12}'', h_{21}'' \rightarrow N_2$

$$v_1 = v_1' + v_1'' \quad I_2 = I_1' + I_2''$$



hence

$$\begin{bmatrix} v_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11}' + h_{11}'' & h_{12}' + h_{12}'' \\ h_{21}' + h_{21}'' & h_{22}' + h_{22}'' \end{bmatrix} \begin{bmatrix} I_1 \\ v_2 \end{bmatrix}$$

h parameters

Summary :-

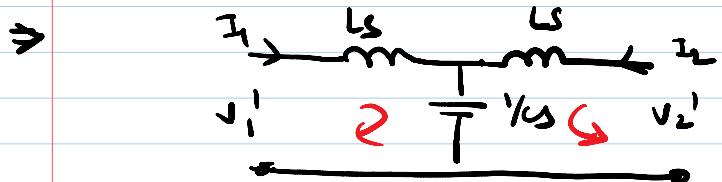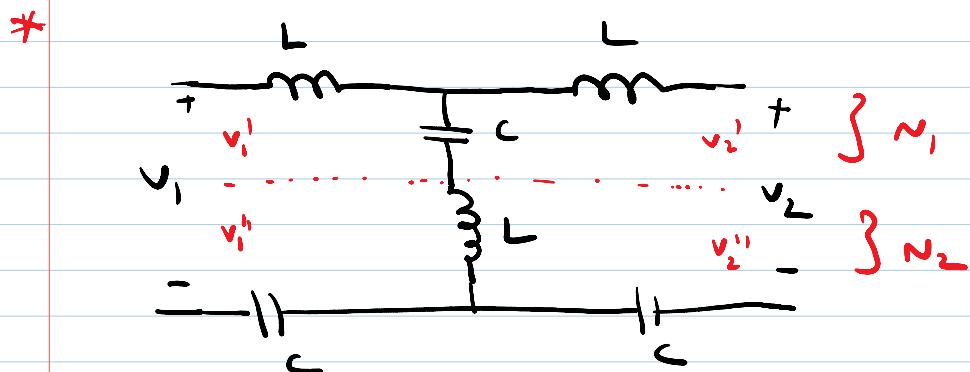- * Cascade connection $\rightarrow ABCD \rightarrow$ product of matrices
- * Parallel connection $\rightarrow Y \rightarrow$ sum of matrices
- * Series " $\rightarrow Z \rightarrow$ "
- * Series - Parallel $\rightarrow h \rightarrow$ "




$$v_1' = \left(Ls + \frac{1}{Cs} \right) I_1 + \frac{1}{Cs} I_2 \quad \rightarrow ①$$

$$-\frac{1}{Cs} I_1 + \frac{1}{Cs} I_2 \rightarrow v$$

$$v_L' = \left(\frac{1}{Cs}\right) I_1 + \left(Ls + \frac{1}{Cs}\right) I_2 \rightarrow ②$$
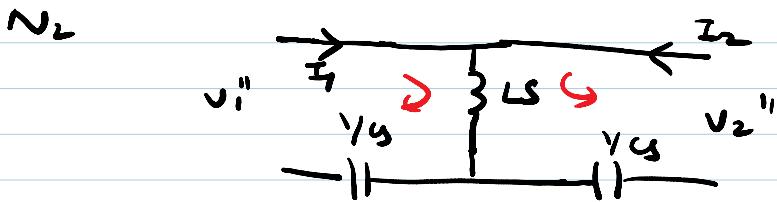
$$Z' = \begin{bmatrix} Ls + \frac{1}{Cs} & \frac{1}{Cs} \\ \frac{1}{Cs} & Ls + \frac{1}{Cs} \end{bmatrix}$$




$$KVL \quad v_1'' = (Ls + \frac{1}{Cs}) I_1 + Ls I_2 \rightarrow ③$$



$$v_2'' = Ls I_1 + (Ls + \frac{1}{Cs}) I_2 \rightarrow ④$$

$$Z'' = \begin{bmatrix} Ls + \frac{1}{Cs} & Ls \\ Ls & Ls + \frac{1}{Cs} \end{bmatrix}$$

$$Z = Z' + Z''$$
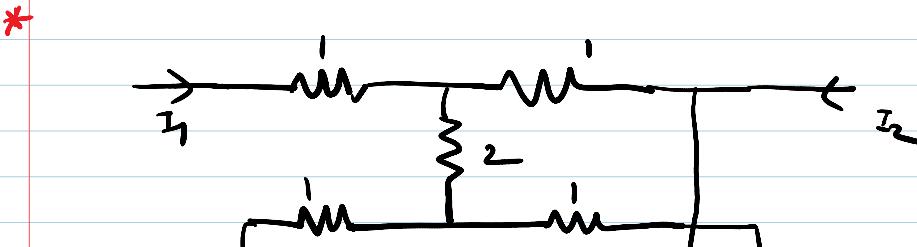
$$\boxed{\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}} = \boxed{\begin{bmatrix} 2Ls + 2/Cs & Ls + 1/Cs \\ Ls + 1/Cs & 2Ls + 2/Cs \end{bmatrix}} = \boxed{Ls + \frac{1}{Cs} \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}}$$



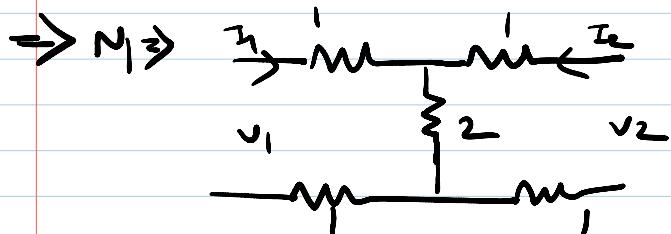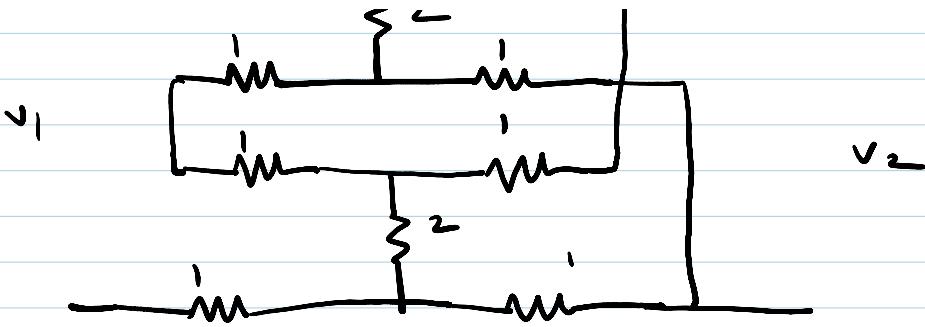

$$v_1 = 4\gamma_1 + 2I_2 \rightarrow \textcircled{1}$$

$$v_2 = 2\gamma_1 + 4I_2 \rightarrow \textcircled{2}$$



Rewrite

$$I_2 = -\frac{1}{2}I_1 + \frac{1}{4}v_2 \quad \textcircled{3} \quad \checkmark$$

Sub $\textcircled{3}$ in $\textcircled{1}$

$$v_1 = 4I_1 + 2\left(-\frac{1}{2}I_1 + \frac{1}{4}v_2\right)$$

$$v_1 = 3I_1 + \frac{1}{2}v_2 \rightarrow \textcircled{4} \quad \checkmark$$

$$h' = \begin{bmatrix} 3 & \gamma_2 \\ -\frac{1}{2} & \frac{1}{4} \end{bmatrix}$$

$$h'' = \begin{bmatrix} 3 & \gamma_2 \\ -\gamma_2 & \frac{1}{4} \end{bmatrix}$$


$$h = h' + h'' = \begin{bmatrix} 6 & 1 \\ -1 & \frac{1}{2} \end{bmatrix}$$

* T → Network :-

Apply KVL

$$v_1 = (z_A + z_c) i_1 + z_c i_2 \quad v_1$$
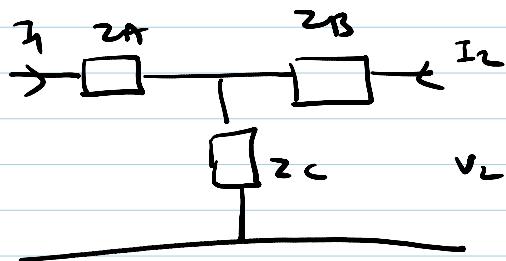
$$v_2 = z_c i_1 + z_B + z_c i_2 \quad v_2$$



$$z_{11} = z_A + z_c \quad)$$

$$z_{12} = z_c \quad)$$

$$z_{21} = z_c \quad)$$

$$z_{22} = z_B + z_c$$

$$z_A = z_{11} - z_{12} = z_{11} - z_{21}$$


$$z_B = z_{22} - z_{21} = z_{22} - z_{12}$$

$$z_c = z_{12} = z_{21}$$

* Pi (Π) Network

Apply KL
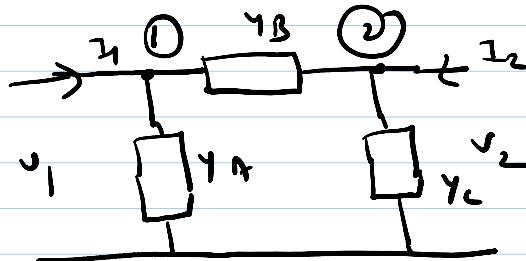
$$i_1 = (\gamma_A + \gamma_B)v_1 - \gamma_B v_2 \quad ①$$



$$i_2 = -\gamma_B v_1 + (\gamma_B + \gamma_C) v_2 \rightarrow ②$$

$$\begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} = \begin{bmatrix} \gamma_A + \gamma_B & -\gamma_B \\ -\gamma_B & \gamma_B + \gamma_C \end{bmatrix}$$

$$\gamma_A = ? \quad \gamma_B = ? \quad \gamma_C = ?$$

$$\gamma_B = -\gamma_{12} = -\gamma_{21}$$

$$\gamma_A = \gamma_{11} + \gamma_{12} = \gamma_{11} + \gamma_{21}$$

$$Y_A = Y_{11} + Y_{12} = Y_1 + Y_2$$

$$Y_C = Y_{22} + Y_{12} = Y_{22} + Y_2$$

* $Z_{11} = 10 \Omega$, $Z_{12} = Z_{21} = 5$, $Z_{22} = 20 \Omega$ find
equivalent T N/W


⇒ Apply KVL
or.

$$Z_{11} = Z_1 + Z_2 = 10$$

$$Z_{12} = Z_2 = 5$$

$$Z_{21} = Z_2 = 5$$

$$Z_{22} = Z_2 + Z_3 = 20$$

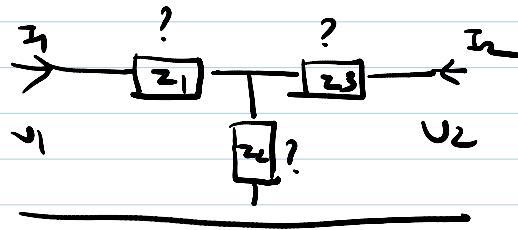

$$Z_1 = ? \quad Z_2 = ? \quad Z_3 = ?$$

Solve $Z_1 = 5 \Omega$

$$Z_2 = 5 \Omega$$

$$Z_3 = 15 \Omega$$