
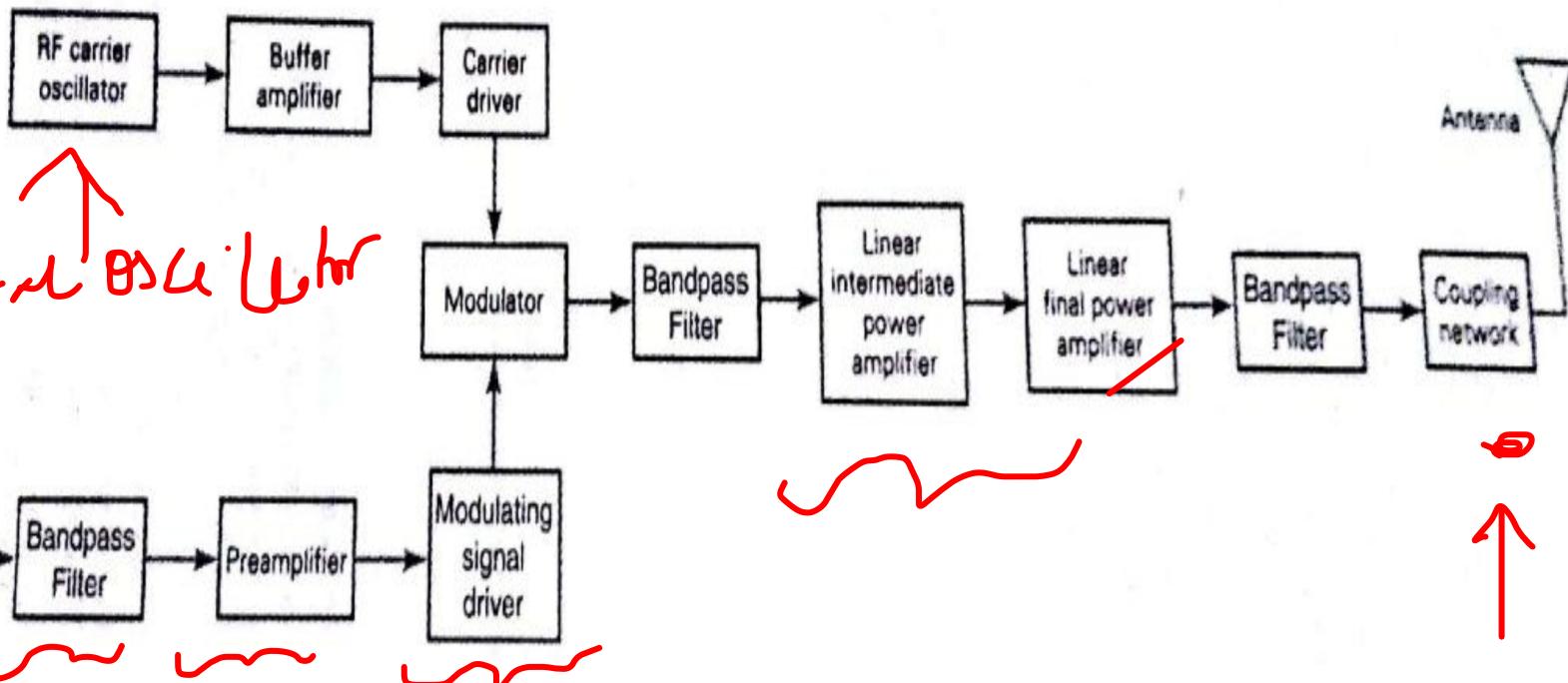


AM DSBFC Transmitter (Low Level)

Carrier

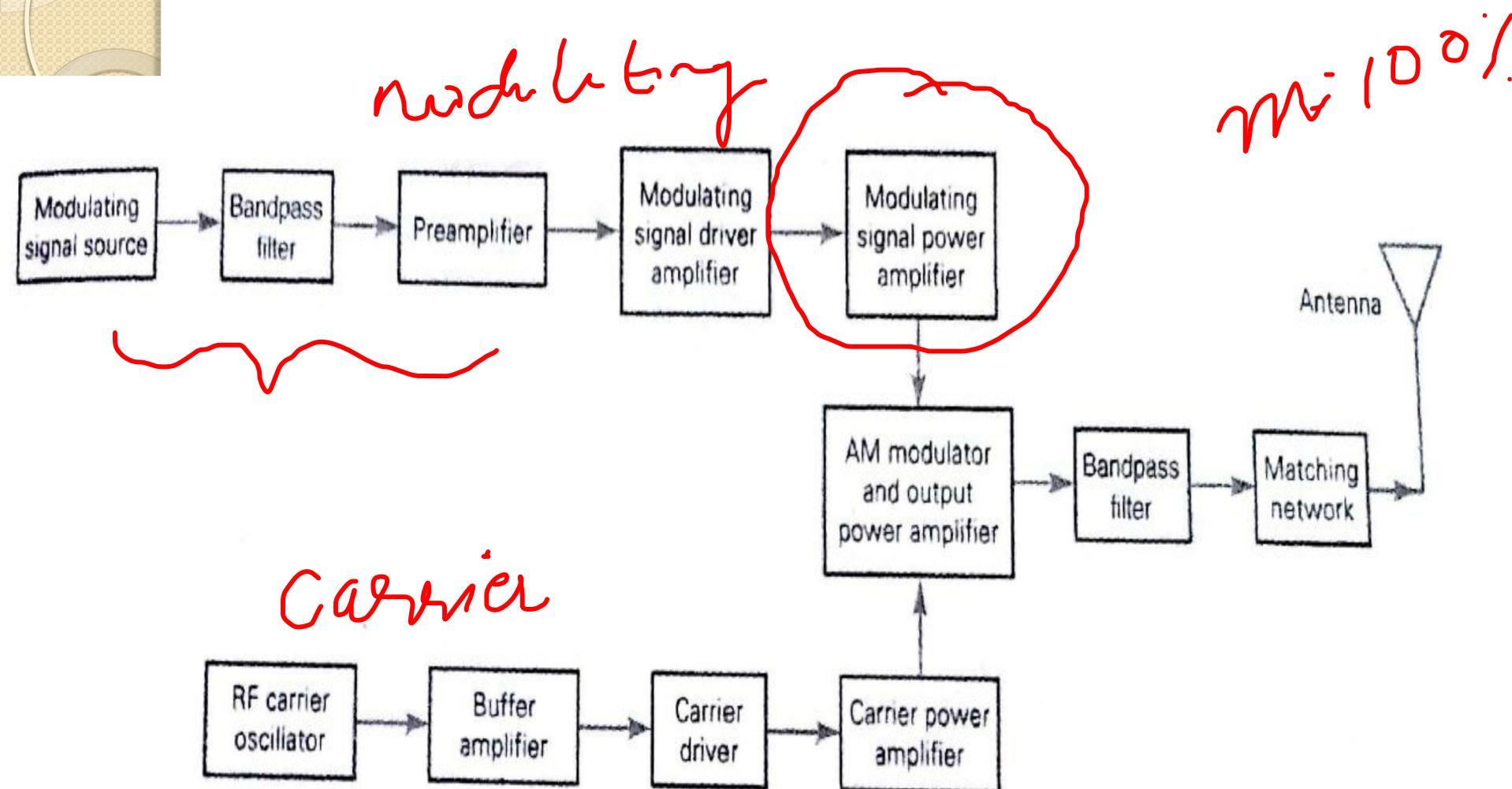

AM DSBFC Transmitter (High Level)




Methods of Detection

Non-Coherent Detection: No need to generate carrier at the receiver for demodulation

Coherent Detection: The carrier is locally generated at the receiver for demodulation.


Simple Diode Detector

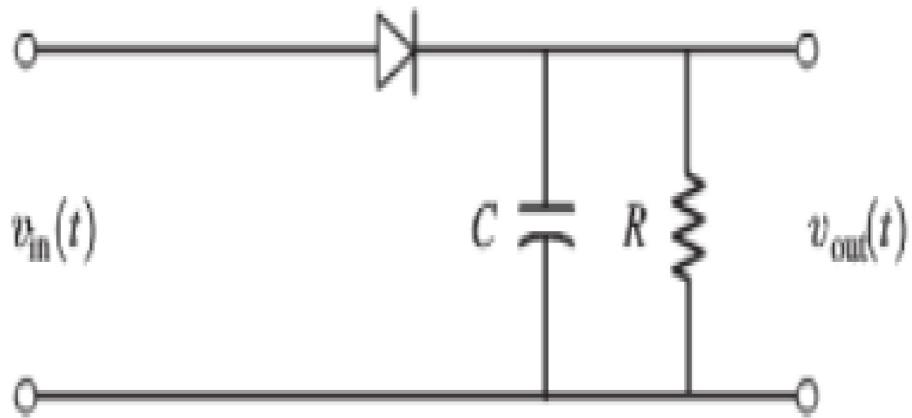

Basic operation: Assume $f_c = 300$ KHz and $f_m = 2$ KHz



- Then there will be frequencies 298, 300, 302 KHz
- The detector will detect many different frequencies
- AM frequencies + AM harmonics + SUM of AM frequencies + DIFF of AM frequencies
- The RC LPF is set to pass only DIFF frequencies

Circuit Diagram


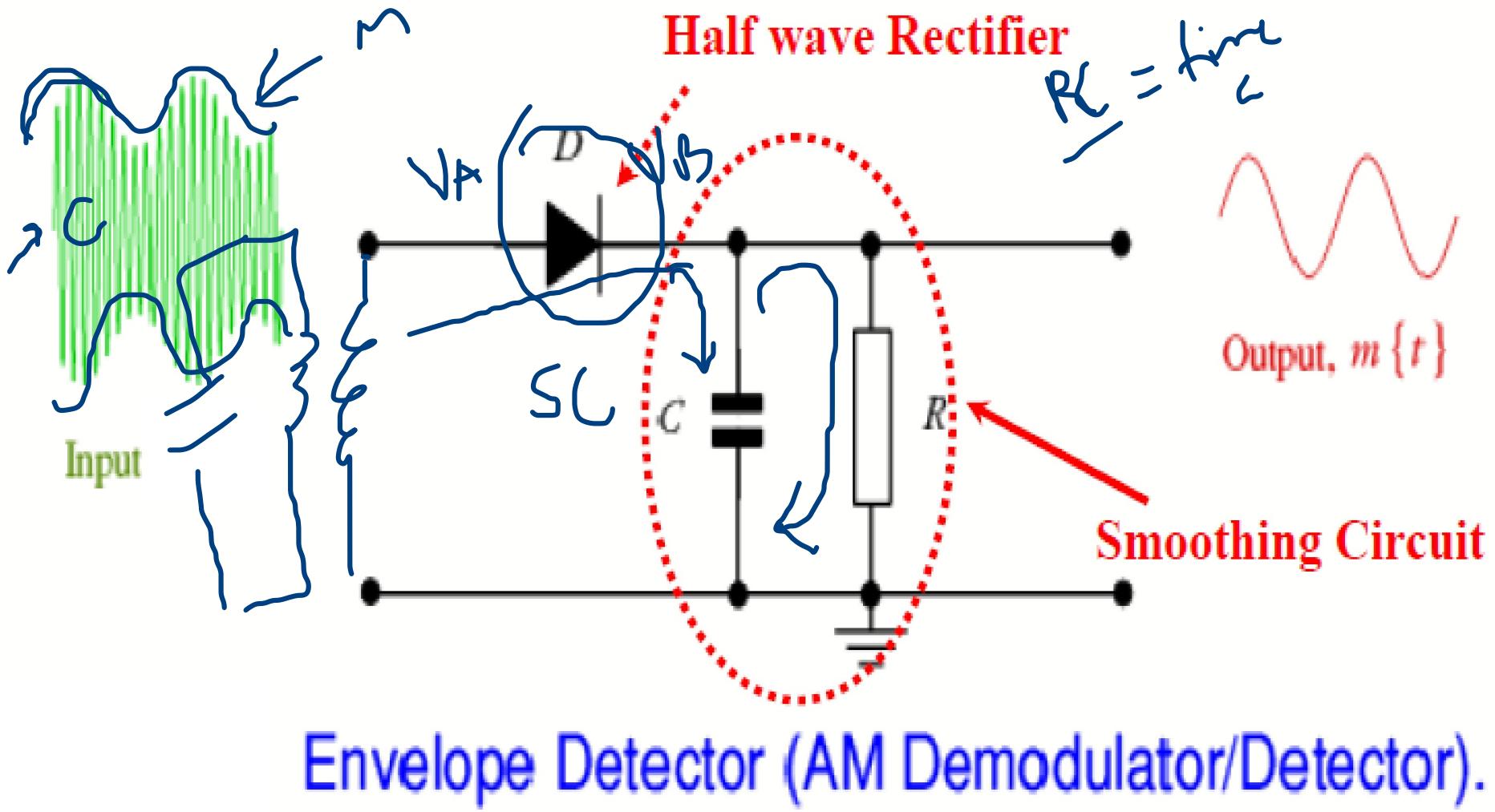


Waveforms at different stages


DSBAM

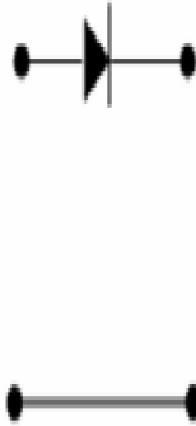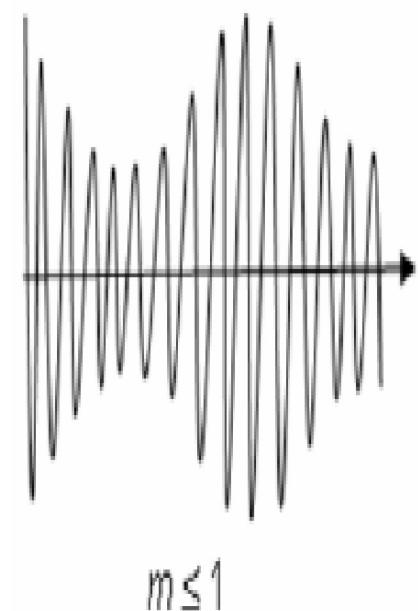

Half wave rectified

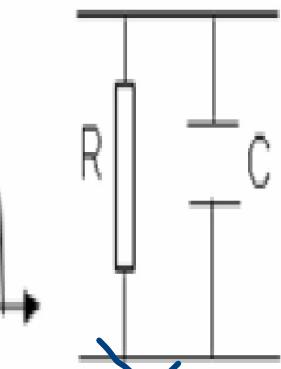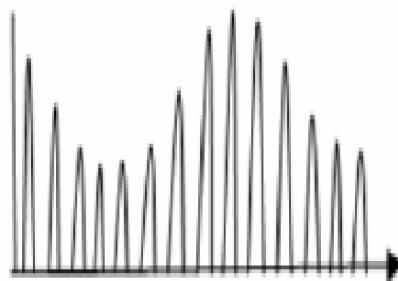


RC $\int m(t) dt$

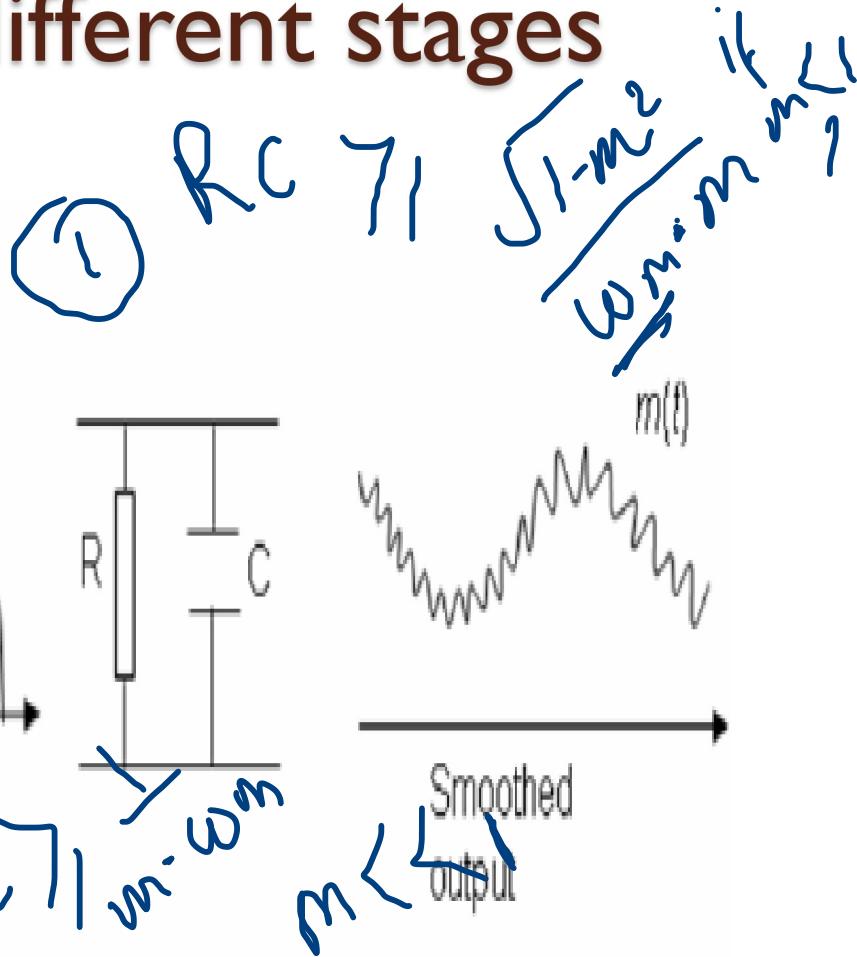





Waveforms

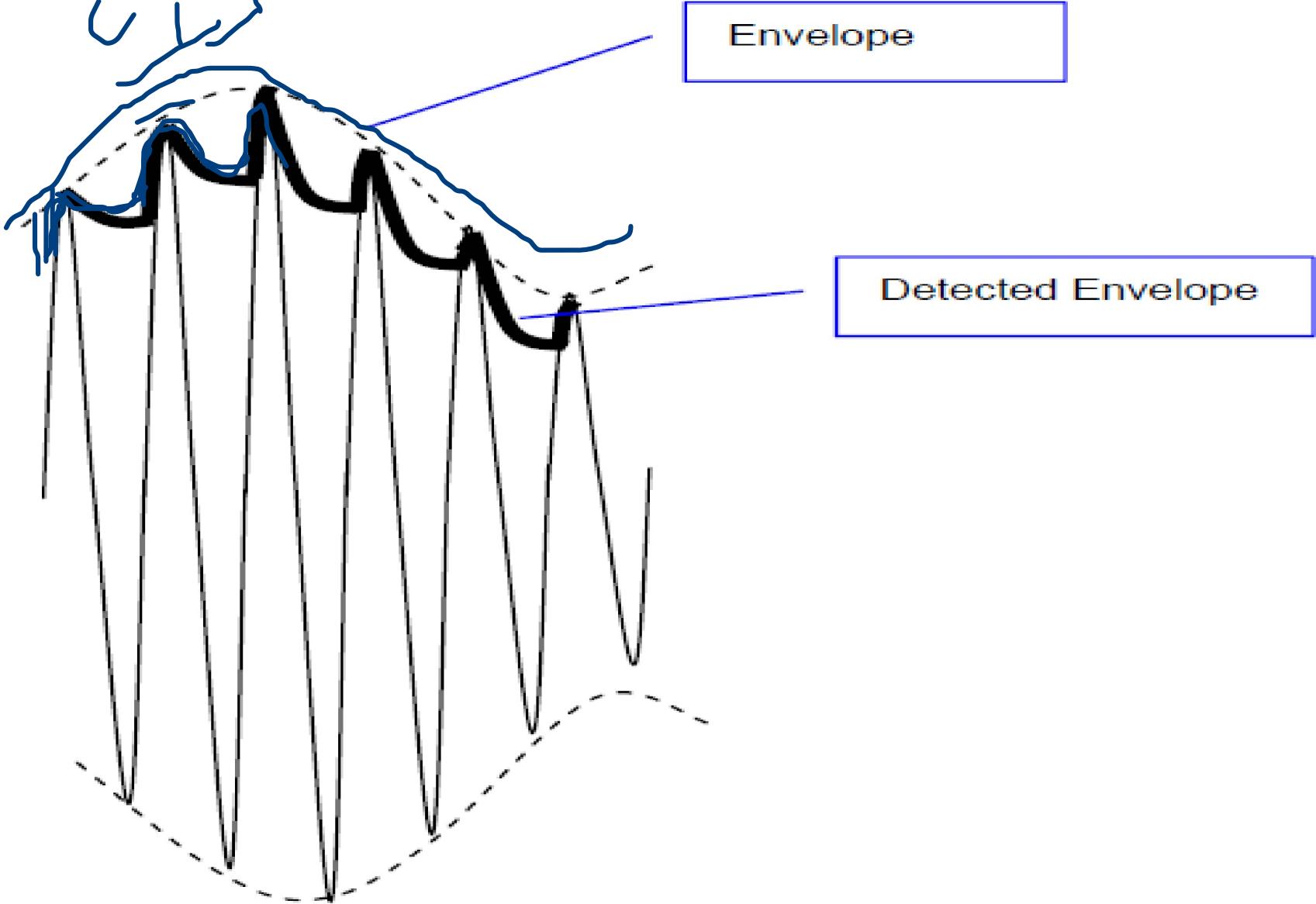

Waveforms (RC time constant is large)

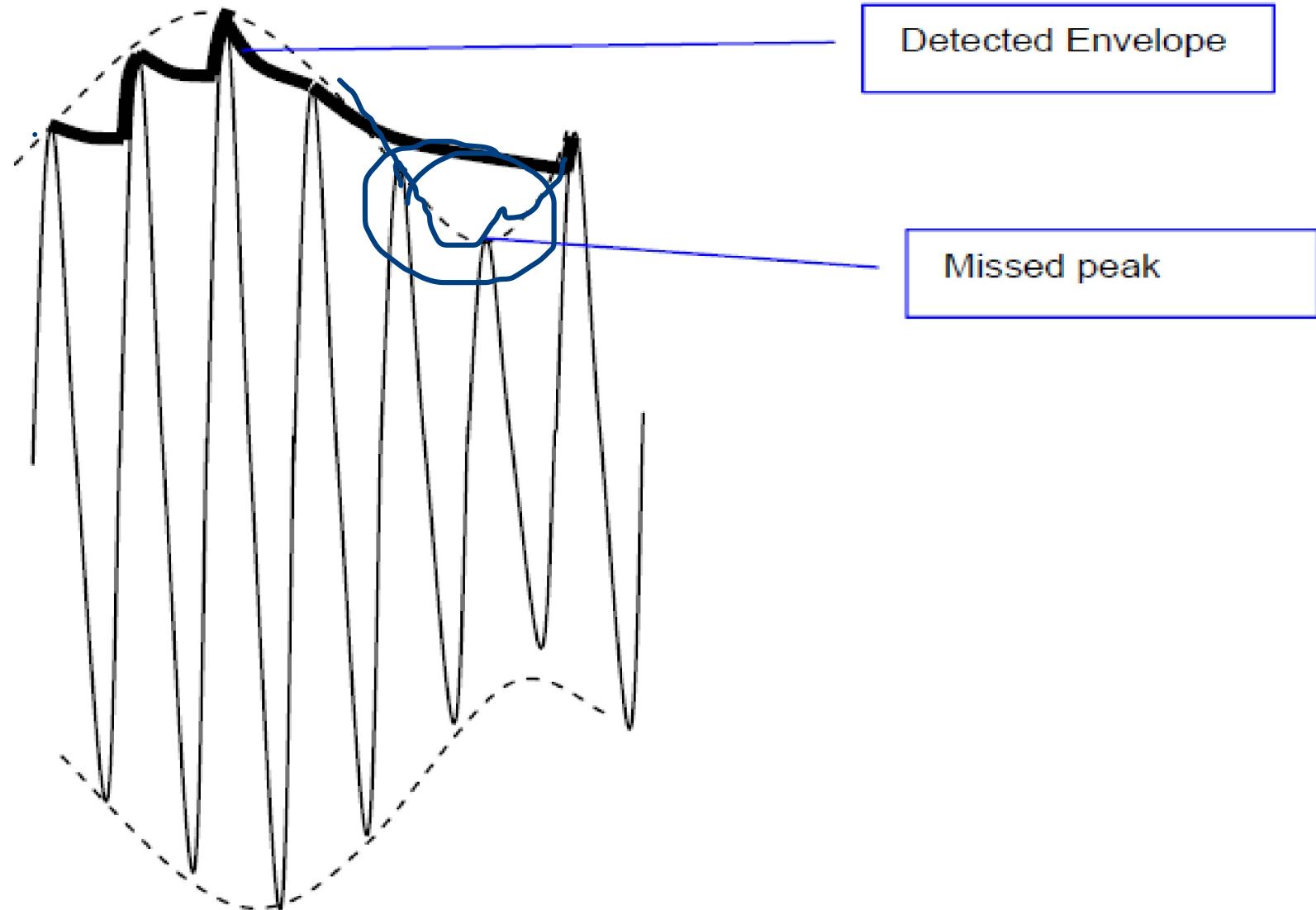

Waveforms (RC time constant is large)

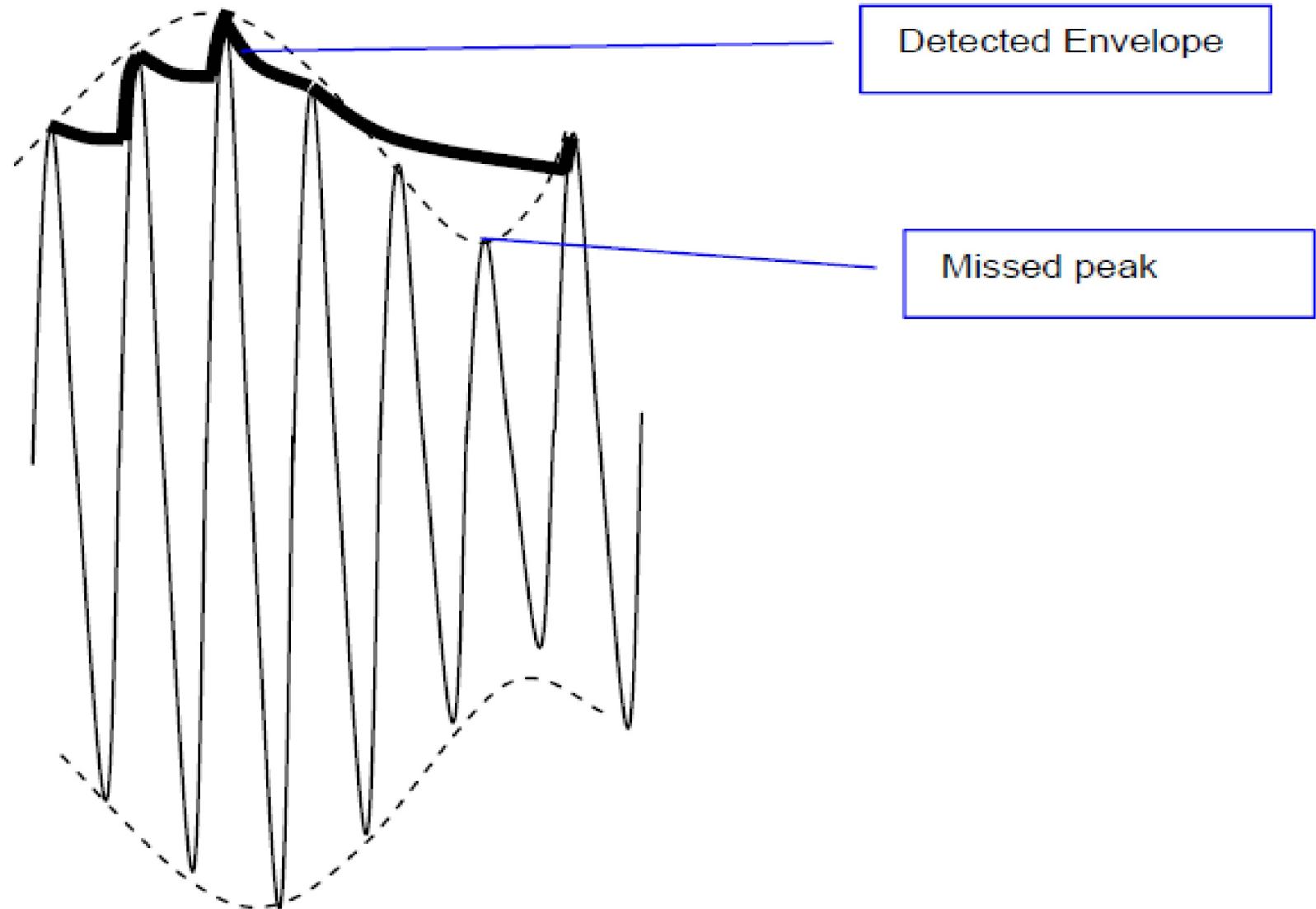



Waveforms (RC time constant is large and too small)

If RC is too small , the carrier wave produced at the output is shown in Fig. 4a.



Fig. 4a.

If RC is too large , the voltages or the signal at the output does not follow the envelope as is Fig. 4b.


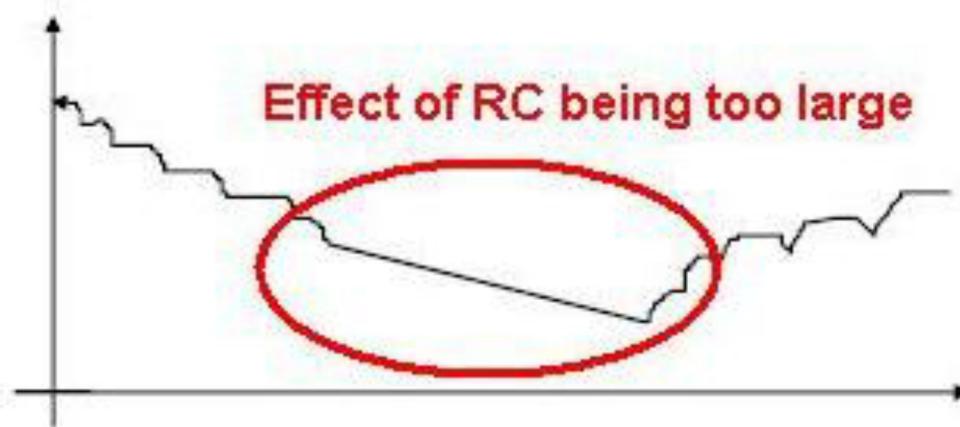
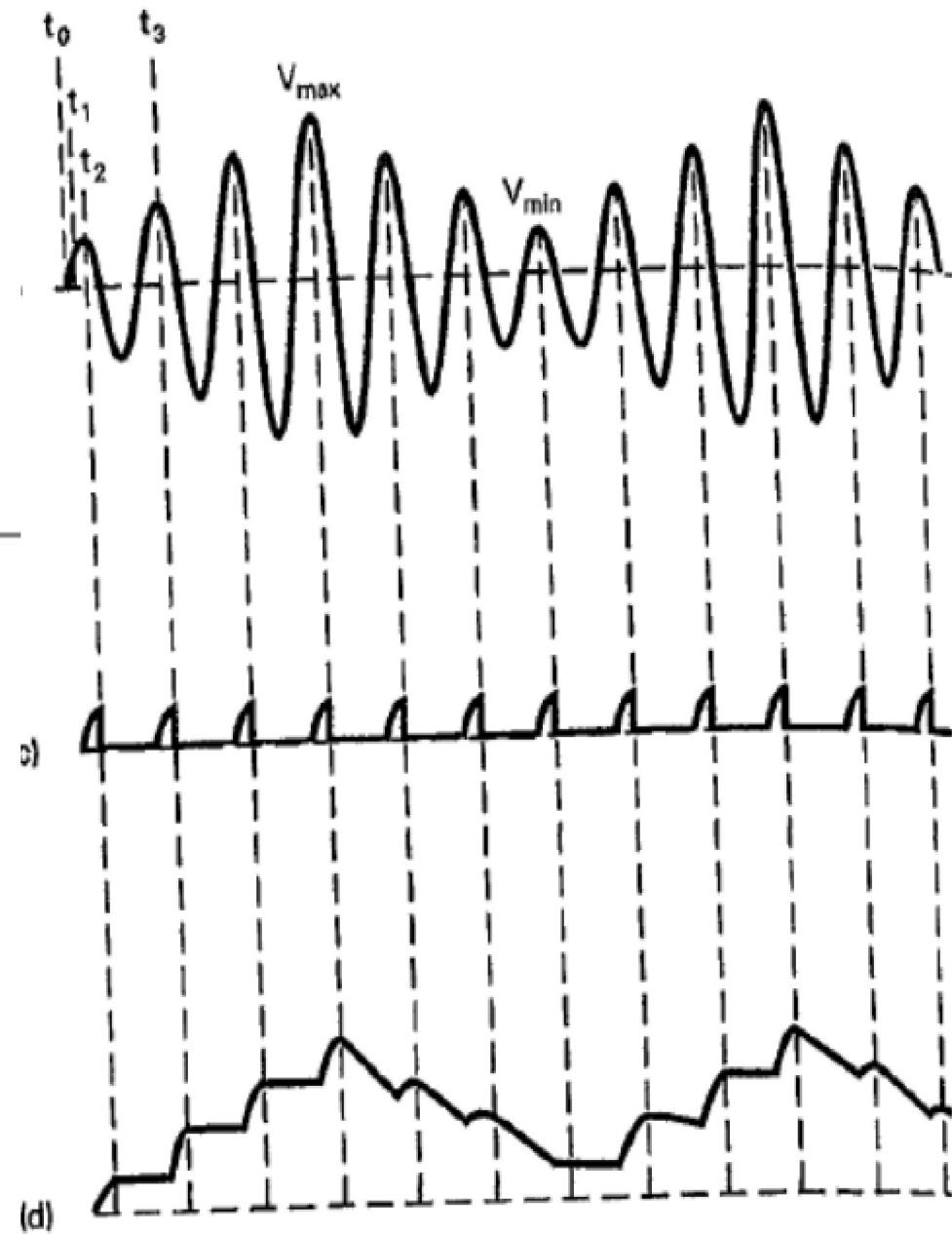


Fig. 4b

Simple Diode Detector Waveforms

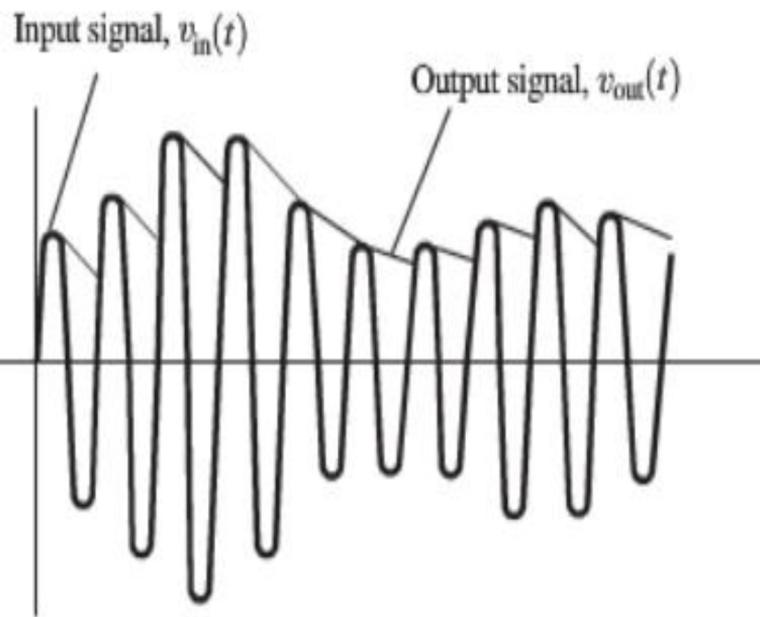


Diode Detector-Distortion


$$RC \approx \frac{1}{m \cdot \omega_m} \sqrt{1 - m^2}$$

- What should be the value of RC?
 - If too low then discharges too fast
 - If too high the envelope will be distorted
 - The highest modulating signal:

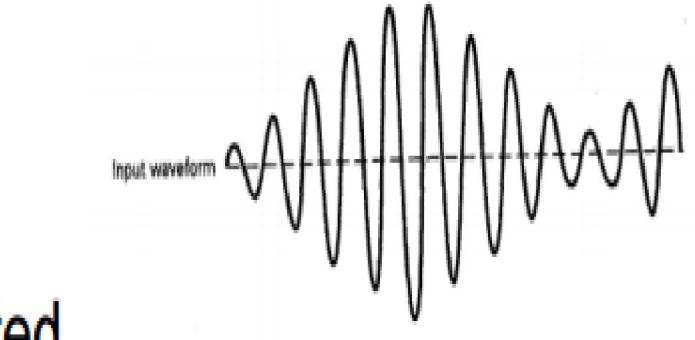
$$f_{m(\max)} = \frac{\sqrt{(1/m^2) - 1}}{2\pi RC}$$



(a) RC too small

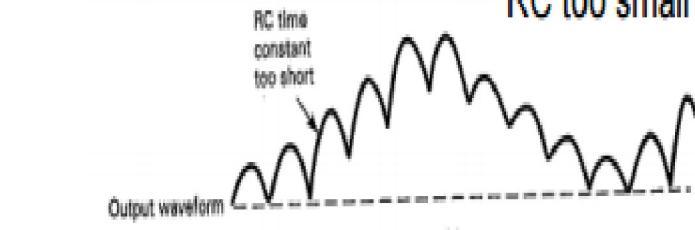

(b)

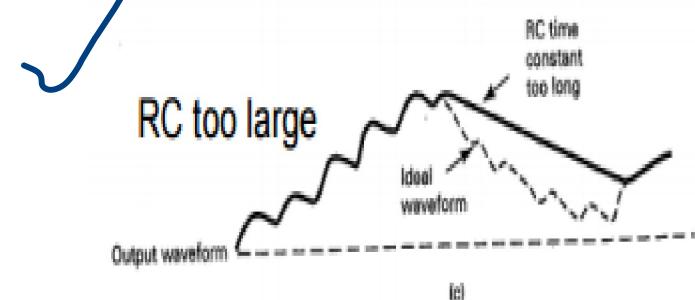

(c)

Practical Diode Detector

