
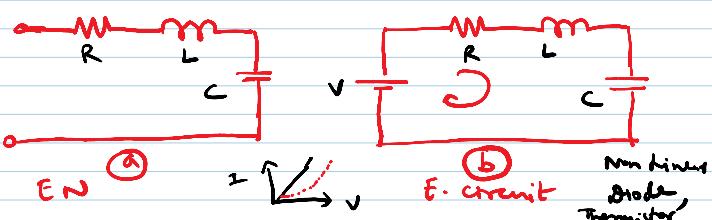



### Network & circuit :-

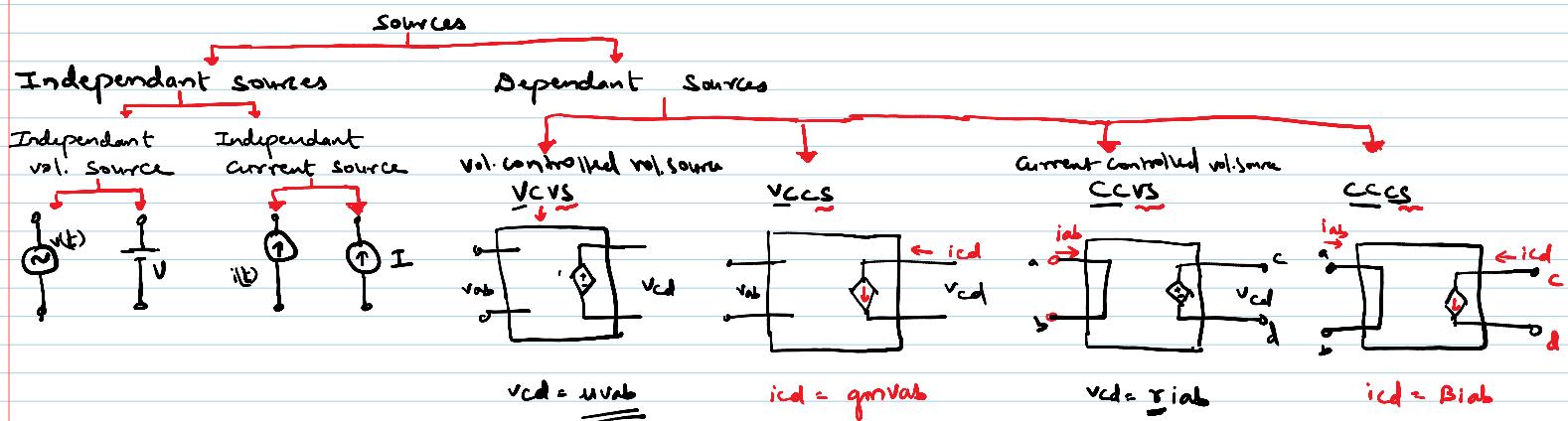

Non linear  
diode  
thermistor




\* KCL  
\* KVL

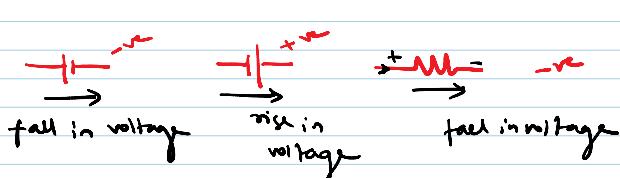

\* Source Transformations



Mesh Analysis:-

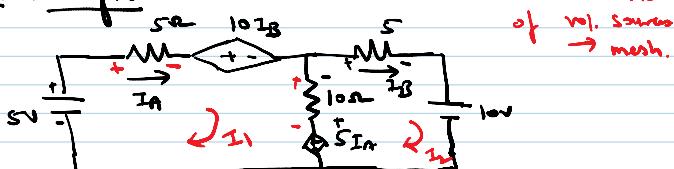

$$I_A = I_1 \\ I_B = I_2$$

$$5 - 5I_1 - 10I_2 - 10(I_1 - I_2) - 5I_A = 0 \quad (1)$$

$$5I_A - 10(I_2 - I_1) - 5I_2 - 10 = 0 \quad (2)$$

Rewriting eqn. (1)

$$5 - 5I_1 - 10I_2 - 10I_1 + 10I_2 - 5I_2 = 0$$

$$-20I_1 = -5 \quad \therefore I_1 = \frac{1}{4} = 0.25A$$


Sub  $I_1$  in eqn ②

$$5I_1 - 10I_2 + 10I_1 - 5I_2 = 10$$

$$15I_1 - 15I_2 = 10$$

$$15(0.25) - 15I_2 = 10$$

$$I_2 = -0.416 A$$

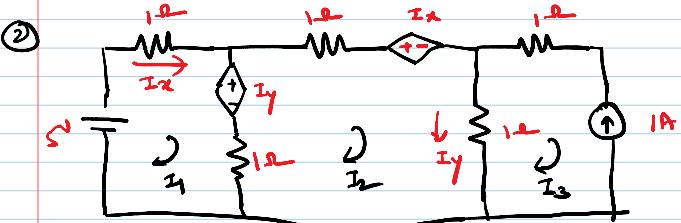

$$\Rightarrow I_3 = -1A \text{ (figure)}$$

$$I_x = I_1$$

$$I_y = I_2 - I_3 = I_2 + 1A \cancel{*}$$

Applying KVL to mesh I & mesh II

$$5 - I_1 - I_y - (I_1 - I_2) = 0 \quad \textcircled{1}$$

$$-(I_2 - I_1) + I_y - I_2 - I_1 - (I_2 - I_3) = 0 \quad \textcircled{2}$$

$$5 - I_1 - (I_2 + 1) - (I_1 - I_2) = 0$$

$$-I_1 - I_2 - I_1 + I_2 = -5 + 1$$

$$-2I_1 = -4$$

$$I_1 = 2 A$$

Sub  $I_1 = 2A$  &  $I_y$  in eqn ②

$$I_2 = 0$$

Prof. Sushma Kadge  
02/06/21

### Supermesh Analysis:-

- We know in mesh analysis, analysis consists of writing mesh equation by KVL in terms of unknown mesh currents.


What is Supermesh?

How to identify supermesh?

Let us consider an example




Let us consider an example

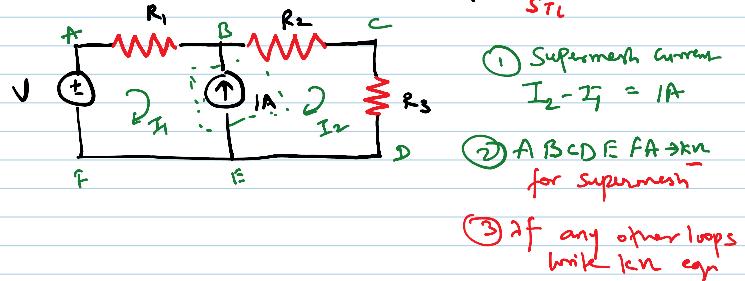

\* Mesh that shares a current source with other meshes (no other current source in outer loop of mesh) → Supermesh

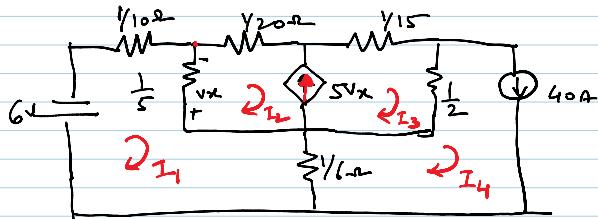\* find currents  $I_1, I_2, I_3$  &  $I_4$  in the network.



⇒  $I_2$  &  $I_3$  form a Supermesh

$$I_3 - I_2 = 5V_x \rightarrow ①$$

$$V_x = \frac{1}{5}(I_2 - I_1) \quad \text{or} \quad -V_x = \frac{1}{5}(I_1 - I_2)$$

$$I_3 - I_2 = \frac{1.5}{5}(I_2 - I_1)$$

$$I_3 = 2I_2 - I_1 \rightarrow ②$$

$$I_4 = 40A \rightarrow ③$$

KVL to Supermesh


$$-\frac{1}{5}(I_2 - I_1) - \frac{1}{20}I_2 - \frac{1}{15}I_3 - \frac{1}{2}(I_3 - I_1) = 0 \quad ④$$

Applying KVL to mesh 1,

$$-6 - \frac{1}{10}I_1 - \frac{1}{5}(I_1 - I_2) - \frac{1}{6}(I_1 - I_2) = 0 \quad ⑤$$

Solve equations 2, 3, 4, 5,

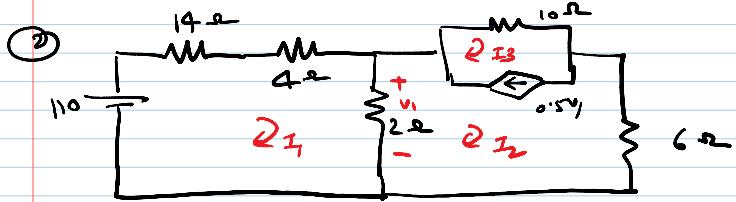$I_1 = 10A$
$I_2 = 20A$
$I_3 = 30A$
$I_4 = 40A$



⇒ Mesh 2 & 3 forming a Supermesh

Current equation for supernode

$$I_3 - I_2 = 0.5V_1 \quad \text{--- (1)}$$

$$V_1 = 2(I_1 - I_2)$$

$$I_3 - I_2 = 0.5V_2(I_1 - I_2)$$

$$I_3 = I_1 \quad \text{--- (2)}$$

KVL eqn for supernode

$$-2(I_2 - I_1) - 10I_3 - 6I_2 = 0 \quad \text{--- (3)}$$

$$-2I_2 + 2I_1 - 10I_1 - 6I_2 = 0$$

$$-8I_1 - 8I_2 = 0$$

$$I_1 = -I_2 \quad \text{--- (4)}$$

KVL for mesh 1

$$110 - 14I_1 - 4I_1 - 2(I_1 - I_2) = 0$$

$$110 - 20I_1 + 2I_2 = 0$$

$$110 + 20I_2 + 2I_2 = 0$$

$$I_2 = -110/22 = -5A$$

$$I_1 = +5A$$


$$I_2 = -5$$

$$I_3 = 5A$$

Node Analysis:- (KCL)

- Assign nodes, then one node  $\rightarrow$  ref. node
- Apply KCL at each node (except ref.)  
Simultaneous eqn.

(3)

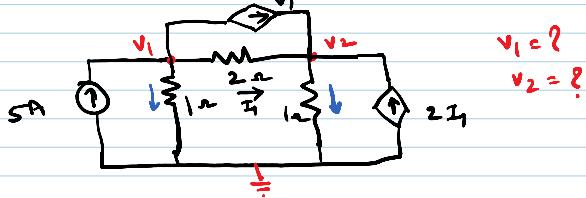

$\Rightarrow$  Applying KCL at node 1 (Assuming unknown branch currents are moving away from node)

$$5 = \frac{V_1}{1} + \frac{V_1 - V_2}{2} + V_1 \rightarrow (1)$$

$$5 = \underline{V_1} + \underline{0.5V_1} - 0.5V_2 + \underline{V_1}$$

$$2.5V_1 - 0.5V_2 = 5 \rightarrow (2)$$

$$V_2 = \frac{V_1 - V_2}{2} + V_1 + 2I_2 \rightarrow (3)$$

$$I_1 = \frac{V_1 - V_2}{2}$$

Sub  $I_1$  in eqn (3)

$$V_2 = \frac{V_1 - V_2}{2} + V_1 + V_1 - V_2$$


$$V_2 = V_1$$

Sub  $V_2 = V_1$  in eqn (2)

$$\boxed{V_1 = 2.5V \\ V_2 = 2.5V}$$
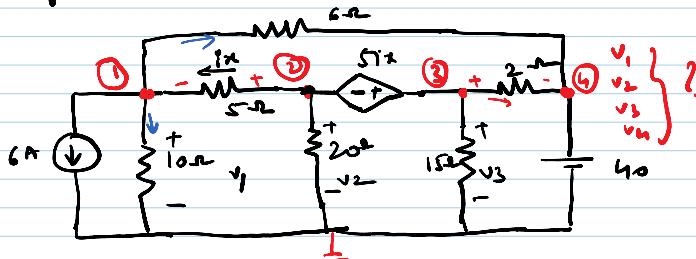
### Supernode Analysis :-

Nodes are connected to each other by voltage sources (not to ref. node)  $\rightarrow$  Supernode




(4)

$$\Rightarrow V_4 = 40V \rightarrow \textcircled{1}$$

Node 2 & 3 form a supernode

$$V_3 - V_2 = 5V \rightarrow \textcircled{2}$$
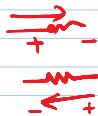
$$\text{As } i_x = \frac{V_2 - V_1}{5} \rightarrow \textcircled{3}$$



$$V_3 - V_2 = V_2 - V_1$$

$$V_3 = 2V_2 - V_1 \rightarrow \textcircled{4}$$

Apply KCL for the Supernode (243)

$$\frac{V_2 - V_1}{5} + \frac{V_2}{2\Omega} + \frac{V_3}{15} + \frac{V_3 - 40}{2} = 0$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{2\Omega} + \frac{2V_2}{15} - \frac{V_1}{15} + \frac{2V_2 - V_1}{2} - 20 = 0$$

$$-\frac{23}{30}V_1 + \frac{83}{60}V_2 = 20 \rightarrow \textcircled{5}$$

Applying KCL at node 1


$$6 + \frac{V_1}{10} + \frac{V_1 - 40}{C} + \frac{V_1 - V_2}{5} = 0 \rightarrow \textcircled{5}$$

$$V_1 = 10V$$


$$V_2 = 20V$$

$$V_3 = 2V_2 - V_1 = 30V$$

$$V_4 = 40V$$

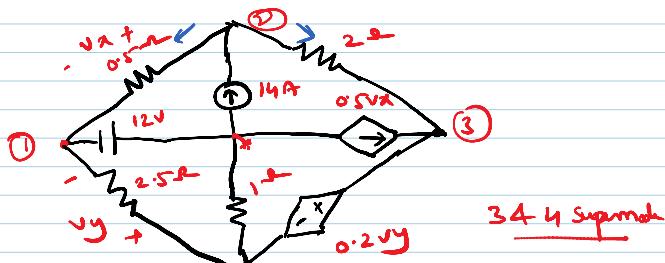

(5)

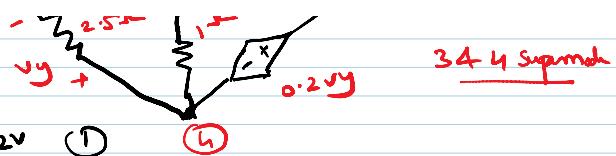

344 Superode

$$\Rightarrow v_1 = -12V \quad (1)$$

KCL at node 2

$$\frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} = 14$$

$$-2v_1 + 2.5v_2 - 0.5v_3 = 14 \quad (2)$$

Node 3 4 u form Superode

$$v_3 - v_4 = 0.2v_4 = 0.2(v_4 - v_1)$$

$$0.2v_1 + v_3 - 1.2v_4 = 0 \rightarrow (3)$$

KCL to the superode (344)

$$\frac{v_3 - v_2}{2} - 0.5v_4 + \frac{v_4 - v_1}{1} + \frac{v_4 - v_1}{2.5} = 0$$

$$\frac{v_3 - v_2}{2} - 0.5(v_2 - v_1) + v_4 + \frac{v_4 - v_1}{2.5} = 0$$

$$0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 = 0 \rightarrow (4)$$

$v_1 = -12V$
$v_2 = -4V$
$v_3 = 0$
$v_4 = -2V$

Prof. Sushma Kadge


03/06/21

### Theorems:-

- 1) Superposition theorem indep. dep. vol. source  $\rightarrow$  s.c.
- 2) Thevenin's theorem dep. I. source
- 3) Norton's theorem
- 4) Maximum power transfer theorem
- 5) Millman's theorem
- 6) Tellegen's theorem
- 7) Reciprocity theorem




Fixed point  
 $V_i$

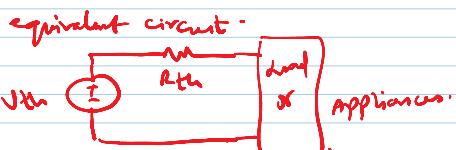

$$V_{th} = V_{oc}$$

$$R_{th} = \text{eqn resistance}$$

Norton theorem:-

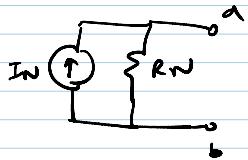

$$I_{IN} = I_{SC}$$

$R_N = \text{eqn. R}_N$

$$R_N = R_{TH}$$

$V_{TH}$ ,  $I_{IN}$ , &  $R_{TH}$


find

$$1) V_{OC} = V_{TH}$$

$$2) I_{SC} = I_{IN}$$

$$3) R_{TH} = R_N = \frac{V_{OC}}{I_{SC}} = \frac{V_{TH}}{I_{IN}}$$

4.2 0.75VA

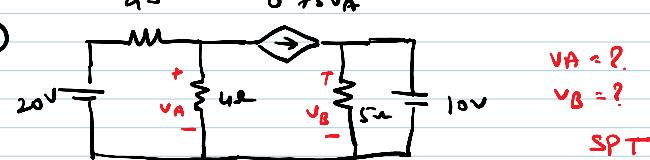


VA = ?

VB = ?

SPT

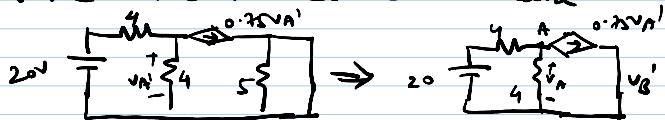→ First we will consider 20V source alone



$$VB' = 0$$

$$VA' = ?$$

Apply KCL at node A

$$\frac{VA' - 20}{4} + \frac{VA'}{4} + 0.75VA' = 0$$

$$1.25VA' = 5$$

$$VA' = 4V$$

$$VB' = 0V$$

10V source is acting



$$VB'' = 10V$$

Applying KCL at node A

$$\frac{VA''}{4} + \frac{VB''}{4} + 0.75VA'' = 0$$

$$V_A'' = 0$$

$$V_B'' = 10V$$

By SPY


$$V_A = V_A' + V_A'' = 4V + 0 = 4V$$

$$V_B = V_B' + V_B'' = 0 + 10V = 10V$$

$$V_A = 4V$$


$$V_B = 10V$$

⑥

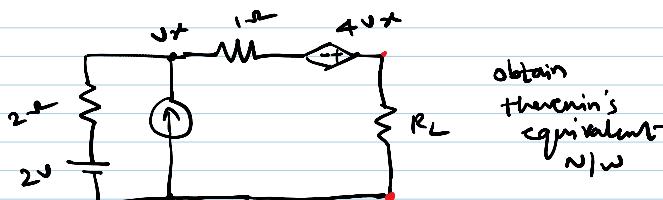

obtain  
thermin's  
equivalent  
N/W

⇒ Find  $V_{th}$  &  $R_{th}$

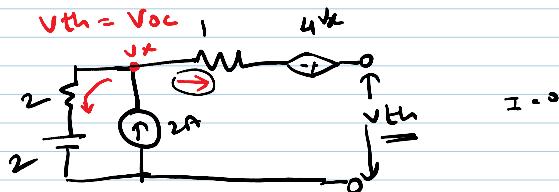

Applying KCL at node  $V_x$

$$\frac{V_x - 2}{2} - 2 = 0$$


$$V_x = 6V$$

$$V_{th} = V_x + 4Vx$$

$$V_{th} = \underline{30V}$$

$$R_{th} = ?$$

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

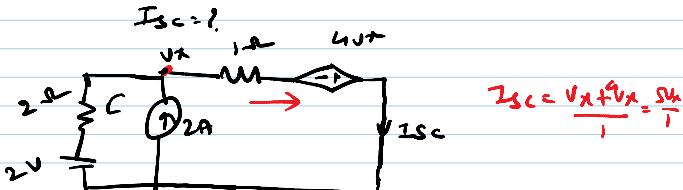

Apply KCL at node  $V_x$

$$\frac{V_x - 2}{2} + \frac{V_x + 4Vx}{1} = 2$$

$$\frac{V_x}{2} + 5Vx = 3$$

$$5.5Vx = 3$$

$$Vx = 3/5.5 = 0.545V$$

$$I_{SC} = \frac{5V}{1} = 5 \times 0.545 = \underline{\underline{2.73 \text{ A}}}$$


$$R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{30}{2.73} = 10.98 \Omega$$




Prof. Sushma Kadge

04/06/21

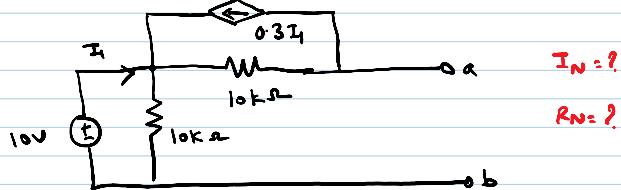⑦ Find Norton equivalent circuit at terminals a & b



→ Short terminals a-b. (I\_N)

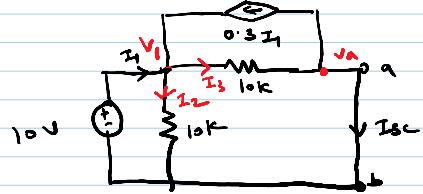

From the figure  $V_1 = 10V$ ,  $V_a = 0V$

KCL at node  $V_1$ ,

$$I_1 - I_2 - I_3 + 0.3I_1 = 0$$

$$I_1 - \frac{V_1}{10k} - \frac{(V_1 - V_a)}{10k} + 0.3I_1 = 0$$

Sub  $V_1$  &  $V_a$

$$I_1 - \frac{10}{10k} - \frac{10}{10k} + 0.3I_1 = 0$$

$$1.3I_1 = \frac{20}{10k}$$

$$\boxed{I_1 = 1.538 \text{ mA}}$$


KCL at node a,

$$I_{SC} = I_3 - 0.3I_1 \quad \therefore I_3 = \frac{V_1}{10k} = \underline{\underline{1 \text{ mA}}}$$


$$I_{SC} = 1 \text{ mA} - 1.538 \times 0.3 \text{ mA.}$$

$$\boxed{I_{SC} = 0.538 \text{ mA}}$$
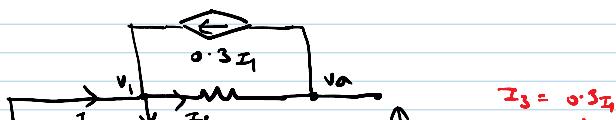
$$R_N = R_{TH} = \frac{V_{TH}}{I_N} = \frac{V_{TH}}{I_{SC}} \quad \checkmark$$



$$I_3 = 0.3I_1$$

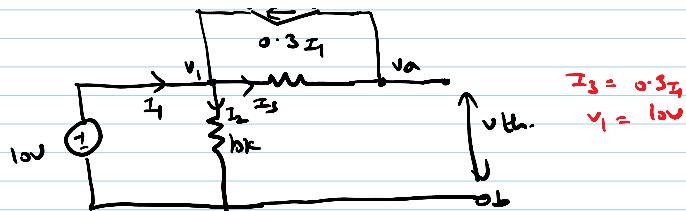


KCL at node 1

$$I_1 + 0.3I_3 - I_2 - I_3 = 0$$

$$I_2 = \frac{v_1}{1k} = 1mA$$



$$I_1 = 1mA$$

$$I_3 = 0.3I_1 = 0.3mA.$$

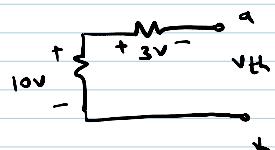


$$v_{th} = 10 - 3 = 7V$$
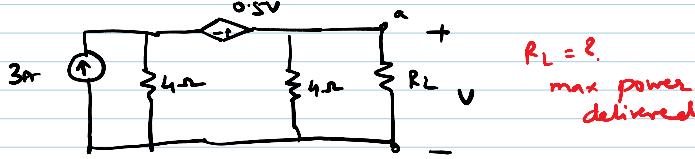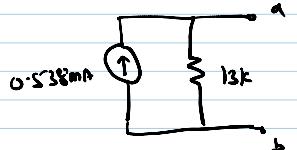
$$R_N = \frac{v_{th}}{I_N} = \frac{7}{0.5 \cdot 2^9} = 13k$$



$$\Rightarrow v_{th} = ? \quad R_{th} = ?$$

open the terminals a-b

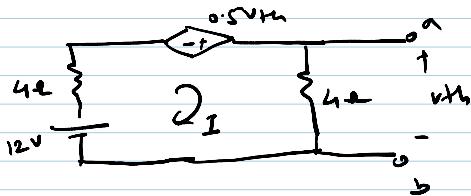

$$v_{th} = 4I$$

KVL to the mesh

$$12 - 4I + 0.5v_{th} - 4I = 0$$

$$12 - v_{th} + 0.5v_{th} - v_{th} = 0$$

$$12 - 1.5v_{th} = 0$$


$$v_{th} = \frac{12}{1.5} = 8V$$

$$12 - 1.5V_m = 0$$

$$V_{th} = \frac{12}{1.5} = 8V$$

$$R_{th} = ?$$

$$\frac{V_{th}}{I_{sc}} \checkmark$$

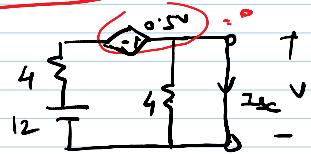

4.2 = Shorted

$$V=0$$

$$0.5V = 0$$



$$I_{sc} = \frac{12}{4} = 3A$$

$$R_{th} = \frac{V_{th}}{I_s} = \frac{8V}{3A} = 2.66\Omega$$

Maximum power delivered to the load,

$$R_L = R_{th} = 2.66\Omega$$



$$P_{max} = I_L^2 \times R_L$$


GRAPH THEORY

- KCL

- KVL

- Theorems  $\rightarrow$  Large  $\rightarrow$  Complicated- Graph theory  $\rightarrow$  Analysis  $\rightarrow$  V & I

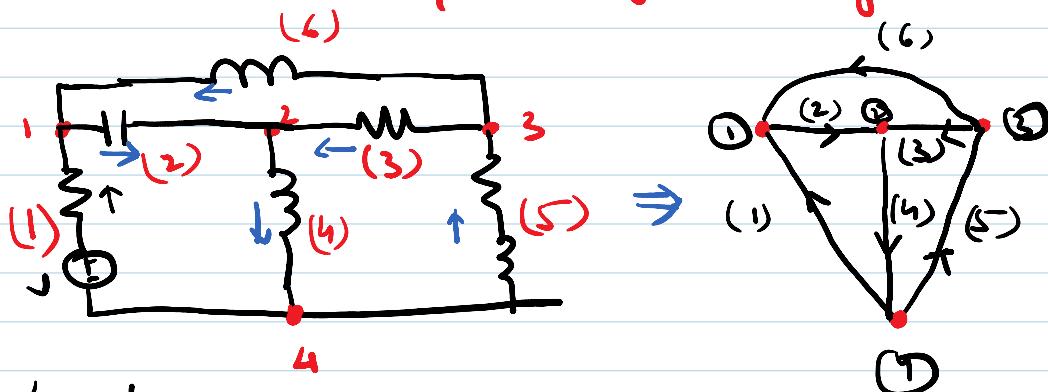
Graph  $\rightarrow$  Collection of nodes & branches  $\rightarrow$   
 they are joined together.




4 nodes  
6 branches

Volt. Source  $\rightarrow$  S.C  
Current Source  $\rightarrow$  O.C


07/06/21

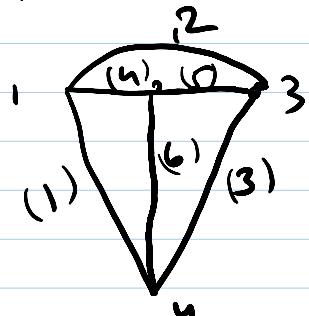

Planar graph

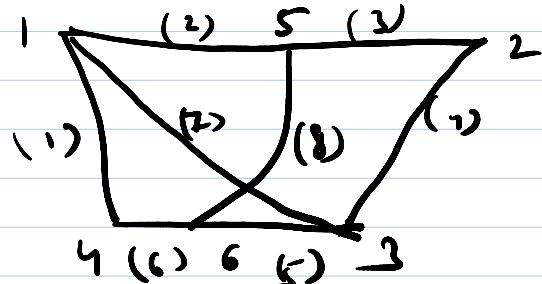



Non-planar graph

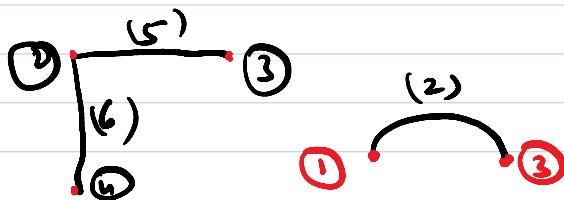

Sub graph

Path



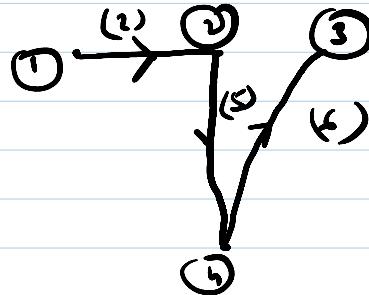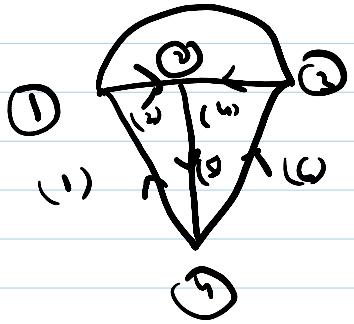


$n = 6$   
 $b = 5$   
 3 twigs  
 3 links

2, 5, 6  $\rightarrow$  6 nodes  $\rightarrow$  path

Tree:-

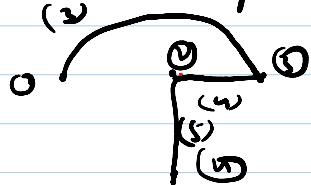- Connected sub graph
- All the nodes of graph
- No loops



Branches of trees  $\rightarrow$  twigs

Trees  $\rightarrow$   $n-1$  twigs ( $n \rightarrow$  nodes)

No. of possible trees =  $\det(AA^T)$

Branches which are not on tree  $\rightarrow$  links/chords  $\rightarrow$  co-tree

$$\text{co-tree} \rightarrow b - (n-1) \text{ links}$$

$$= 6 - (6-1)$$

$$= 3 \text{ links}$$

(Complement of tree)

Incident matrix:- It gives us the information

about which branch is incident on which node,  
 & what are its orientation w.r.t to nodes.


Information is written in form of matrix  
 which is known as Incident matrix

Complete Incident Matrix ( $A_b$ )

$a_{nk} = 1$  if branch  $k^{th}$  is incident at node  $n^{th}$  & its oriented away from the node  $n$ .

= -1 " " " " " "

- towards the node

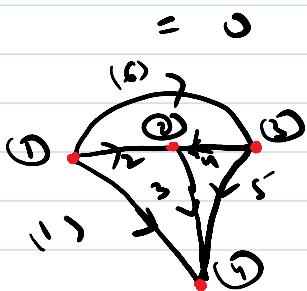

Not incident

nodes ↓	Branches →					
	1	2	3	4	5	6
1	1	1	0	0	0	1
2	0	-1	1	-1	0	0
3	-1	0	0	1	1	-1
4	-1	0	-1	0	-1	0

$$A_a = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \\ -1 & 0 & 1 & 0 & -1 & 0 \end{bmatrix}$$

$\Sigma E R O$  = sum of each columns

$$A = ?$$

Reduced Incidence matrix ( $A$ ) → Eliminate anyone n

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$


H.W. No. of possible trees =  $\det(\underline{A} \cdot \underline{A}^T) = \underline{16}$

loop matrix or circuit matrix

Matrix gives us information about which branches constitute loop or circuit.

$b_{nk} = 1$  if branch 'k' is in loop & their orientation coincide

-1	"	"	"	"	donot
0	"	"	Not in loop		

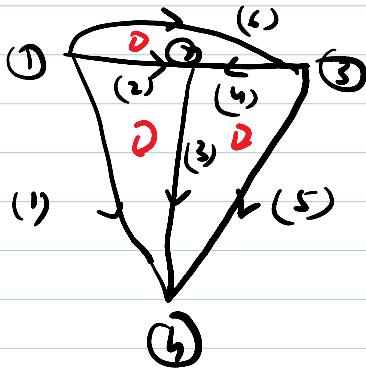


Loops ↓

	1	2	3	4	5	6
Loop 1:	1	2	3	0	0	0
Loop 2:	0	0	-1	-1	1	0
3:	0	-1	0	1	0	1
4 =	-1	1	0	-1	1	0
5 =	-1	0	0	0	1	1
6 =	0	-1	-1	0	1	1
7 =	-1	0	1	1	0	0

Prof. Sushma Kadge

08/06/21

### Ticset matrix (Fundamental circuit)

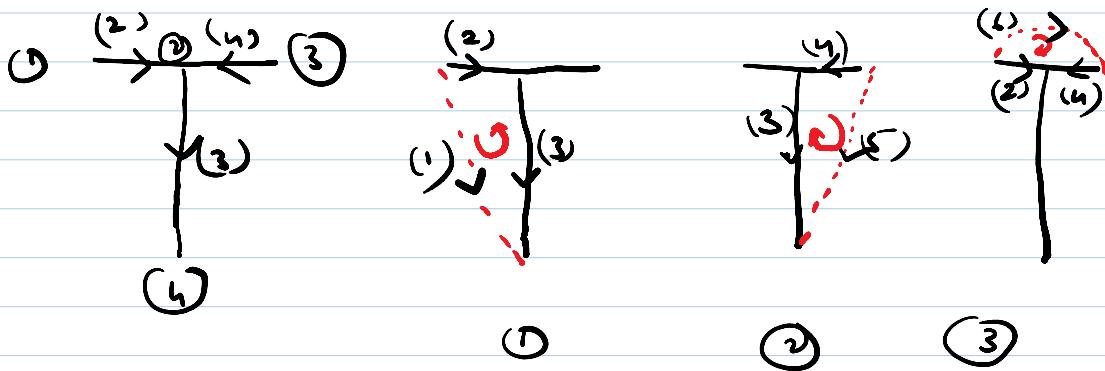

Ticset 1: (1, 2, 3)

Ticset 5: (5, 3, 4)

Ticset 6: (6, 2, 4)

$$\begin{aligned} \text{no. of ticsets} &= b - n + 1 \\ &\leq 6 - 4 + 1 \\ &= 3, \end{aligned}$$

$$B = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & -1 & -1 & 0 & 0 & 0 \\ 5 & 0 & 0 & -1 & -1 & 1 & 0 \\ 6 & 0 & -1 & 0 & 1 & 0 & 1 \end{bmatrix}$$

Rearrange

$$B = \begin{bmatrix} \text{Twigs} & \text{Links} \\ 2 & 3 & 4 & 1 & 5 & 6 \\ -1 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 1 & 0 \end{bmatrix}$$

$$B = \begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 1 & 0 \\ -1 & 0 & 1 & 0 & 0 & 1 \end{bmatrix}$$

$$B = [B_L : B_U] = [B_L : U]$$

unit matrix

$A_a \rightarrow$  Complete incident matrix  
 $A \rightarrow$  Reduced  
 $B_a \rightarrow$  Loop matrix  
 $B \rightarrow$  Tie set matrix

or  
 or  
 or  
 or

or orthogonal

$$A_a B_a^T = 0 \quad \text{or} \quad B_a A_a^T = 0$$

$$AB^T = 0 \quad \text{or} \quad B^T A = 0$$

Cutset matrix :-

The removal of set of branches results in cutting the graph into parts.


$q_{nx} = 1$  if branch 'k' is in cutset 'n' & orientations coincide


-1 " " " don't coincide

0 " " " is not in the cutset


$$Q_a = [ ]$$

Fundamental cutset matrix ( $q$ )

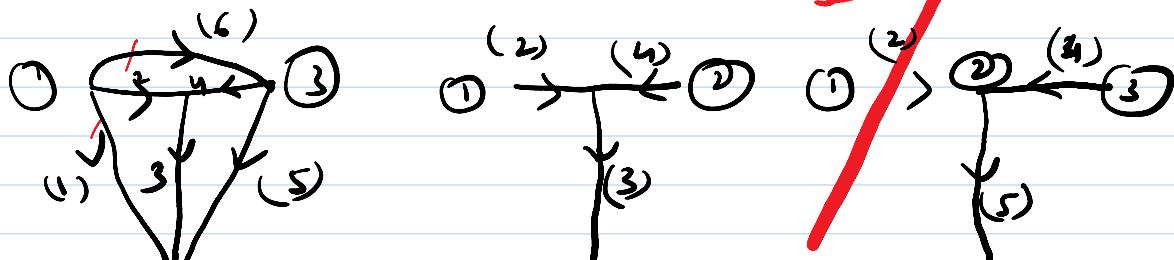

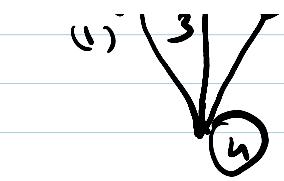

$f_{\text{subset } 3} : \{3, 1, 5\}$

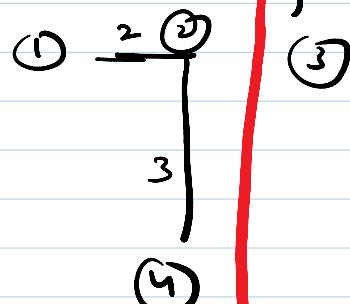

$f_{\text{subset } 2} : [2, 1, 6]$

$f_{\text{subset } 4} : [4, 5, 6]$

$$g = \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \end{matrix}$$


$$g = [g_t : g_x] = [v : g_x]$$

Relationship between  $B$  &  $g$  matrix


orthogonal

$$g_a B_a^T = 0 \quad \text{or} \quad B_a g_a^T = 0$$
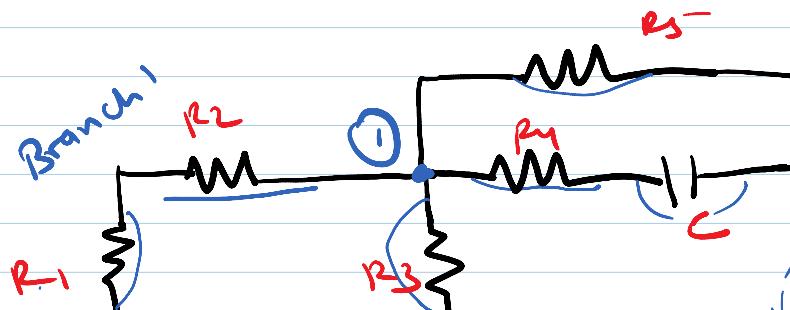
$$g B^T = 0 \quad \text{or} \quad B g^T = 0$$



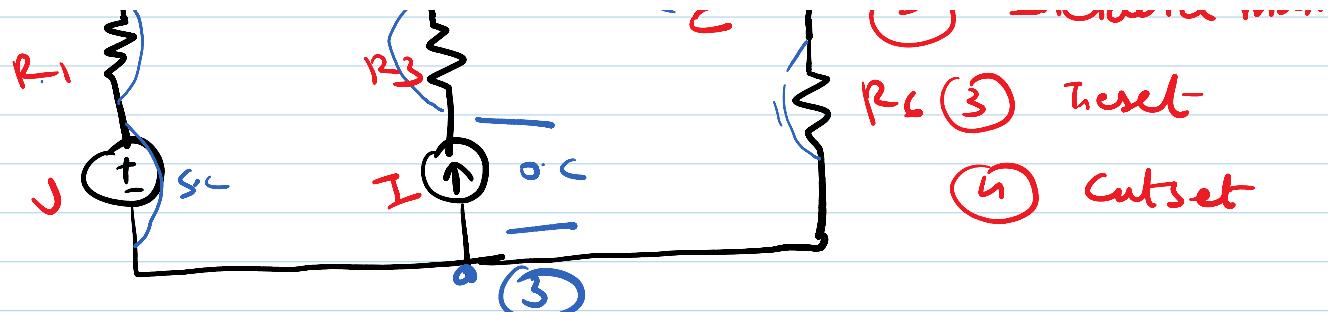
- ① Draw oriented graph
- ② Incidence matrix
- R, L, Tared



① Replace  $R, L, C \rightarrow$  line segments

② " Vol. Source  $\rightarrow S.C$   
I. Source  $\rightarrow O.C$

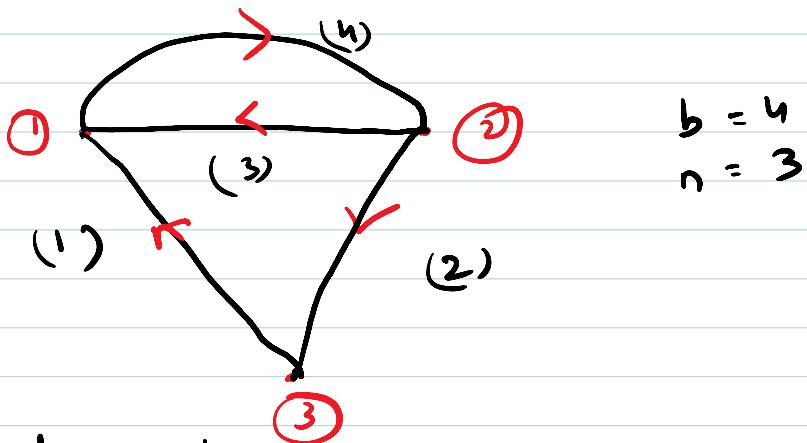③ Assume directions of branches current  
All the nodes & branches  $\rightarrow$  Number



$$b = 4 \\ n = 3$$

④ Complete incidence matrix

$$A_a = \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & 0 & -1 & 1 \\ 0 & +1 & +1 & -1 \\ 1 & -1 & 0 & 0 \end{bmatrix}$$

Reduced Incidence matrix  $2 \in RD$

$$A = \begin{bmatrix} -1 & 0 & -1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

Prof. Sushma Kadge  
09/06/21(10:30am)

⑤ Tieset matrix :-


1) Select any Tree



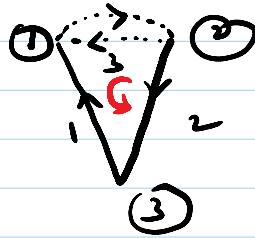1) Select any Tree

$$\begin{array}{l} \text{Twigs} \rightarrow 1, 2 \\ \text{links} \rightarrow \underline{3}, \underline{4} \end{array}$$


$$\begin{array}{l} \text{Tieset } 3 \rightarrow 3, 1, 2 \\ 4 \rightarrow 4, 1, 2 \end{array}$$



$$B = \begin{bmatrix} 1 & 2 & 3 & 4 \\ 3 & -1 & -1 & 1 \\ 4 & 1 & 1 & 0 \end{bmatrix}$$

$$\begin{array}{l} BT : u \\ BT : BL \end{array}$$


② f-cutset matrix ( $G$ ):

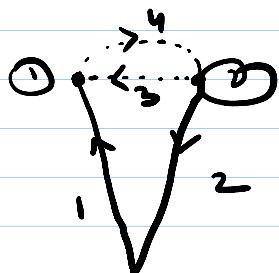

f-cutset 1 : [1, 3, 4]

f-cutset 2 : [2, 3, 4]
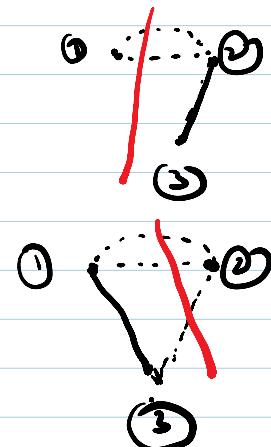
$$G = \begin{bmatrix} 1 & 0 & 1 & -1 \\ 2 & 0 & 1 & -1 \end{bmatrix}$$





$$A = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

graph = ?

⇒ Complete incidence matrix
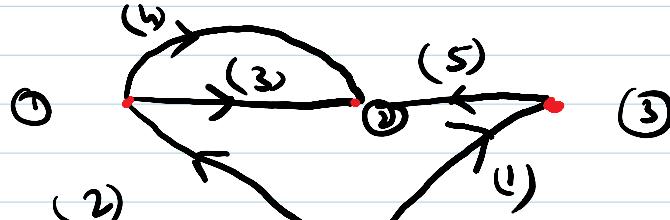
$$A_g = \begin{array}{c} \begin{array}{ccccc} 1 & 2 & 3 & 4 & 5 \leftarrow \text{Branches.} \end{array} \\ \begin{array}{c} 1 \\ 2 \\ 3 \\ 4 \\ \uparrow \text{nodes} \end{array} \end{array} \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \\ 1 & +1 & 0 & 0 & 0 \end{bmatrix} \quad 2 \in R_0$$



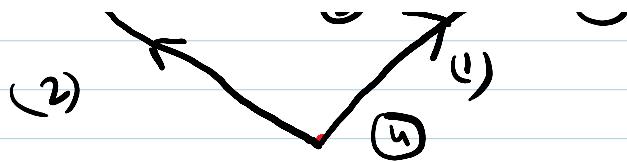

Duality :- (planer N/W)

Two N/Ws  $\rightarrow$  dual of each other

Two graphs  $\rightarrow$  "

Conversion for Dual circuits

loop basis

Current

Resistance

Inductance

Branch current

Mesh

S.C

Parallel path

node basis

Voltage

Conductance

Capacitance

Branch voltage


Node

O.C


Series path

Construction of a dual N/W :-



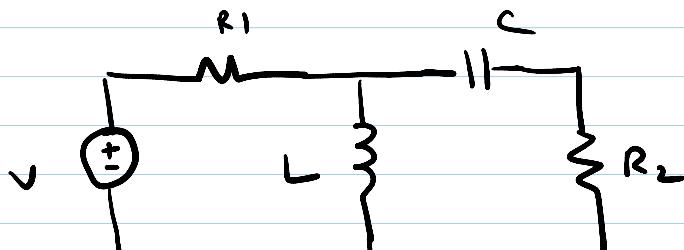
- 1) Place a dot in each mesh of a N/W
- 2) ' ' ' ' outside N/W  $\rightarrow$  reference node
- 3) Connect all internal dot in adjacent
- 4) ' ' ' ' " to the external dot
- 5) Clockwise current  $\rightarrow$  +ve polarity
- 6) Voltage rise in dir<sup>n</sup> of a Clockwise current  
correspond current flowing towards the  
dual indep. node.



Dual N/W ?


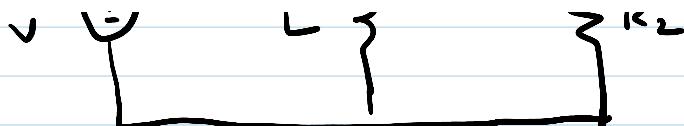


→

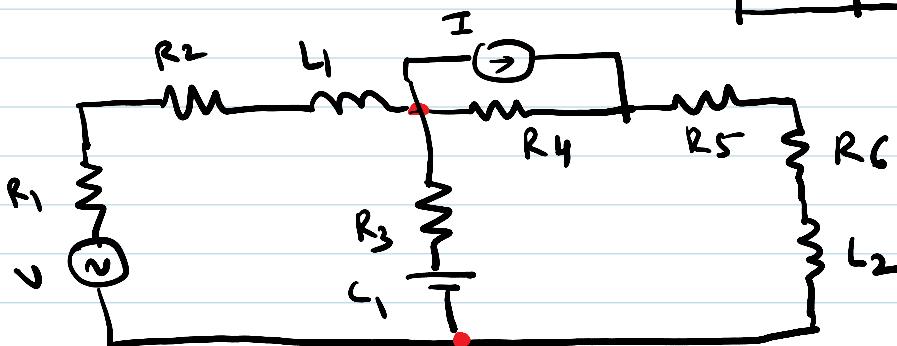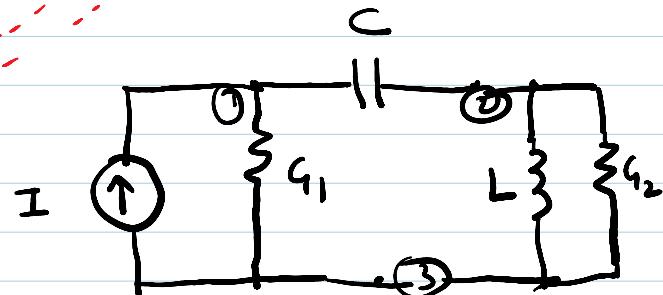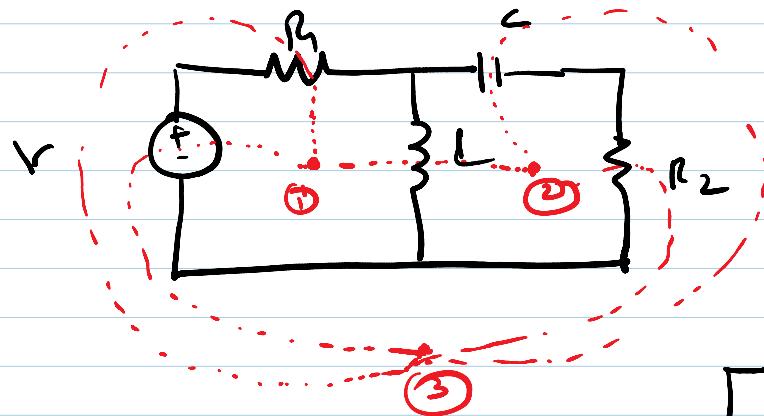

- ① Oriented graph
- ② Incidence matrix
- ③ T-sets matrix
- ④ Cutset matrix

→

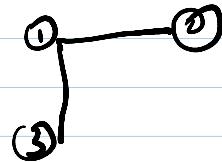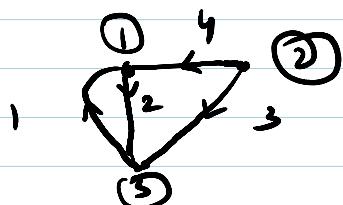

Complete incidence matrix ( $A_a$ ):


$$A_a = \begin{array}{c|cccc} & 1 & 2 & 3 & 4 \\ \hline 1 & -1 & 1 & 0 & -1 \\ 2 & 0 & 0 & 1 & 1 \\ 3 & 1 & -1 & -1 & 0 \end{array}$$

$\xrightarrow{\text{2 E R10}}$

Incidence matrix :-

$$A = \begin{bmatrix} -1 & 1 & 0 & -1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$


Tree-set matrix.

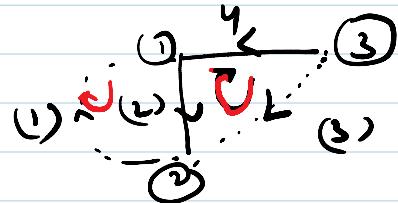

$$B = \frac{1}{3} \begin{bmatrix} 1 & 2 & 3 & 4 \\ 1 & 1 & 0 & 0 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

Cutset matrix  $\Omega$  =
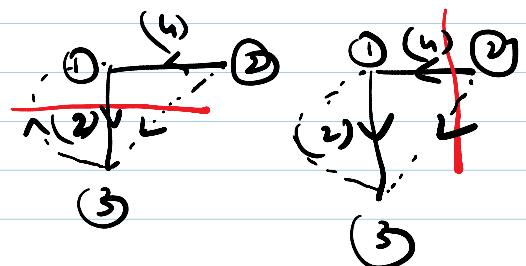
$$\Omega = \frac{1}{4} \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$



Prof. Sushma Kadge

09/06/21 (2:15pm)

\* KVL, KCL, Network equilibrium equation

KVL.

$$\sum_{k=1}^b v_k = 0 \quad k^b \rightarrow \text{branch}$$

$$\sum_{k=1}^b b_{hk} v_k = 0$$

$$\boxed{BV_b = 0}$$

$v_b \rightarrow \text{column vector}$

KCL :-

$$\sum i_k = 0$$

b

$$\sum_{k=1}^n a_{ik} i_k = 0$$

$$\downarrow$$

$$A_a I_b = 0$$

$I_b \rightarrow$  column vector

$$A I_b = 0$$


$$Q I_b = 0$$

$$v_b = Q^T v_t$$

$$I_b = B^T I_L$$

Relation between

## Network Equilibrium equation (KVL)

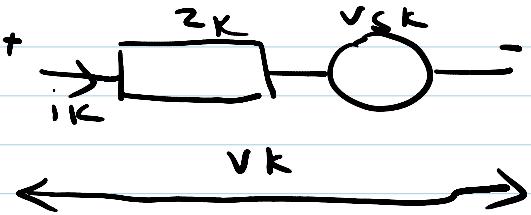

$$V_k = Z_k i_k - V_{s_k} \quad k = 1, 2, 3, \dots, b$$

$$V_b = Z_b i_b - V_s$$

$$B V_b = 0 \quad \text{KVL}$$

$$\underbrace{B [Z_b i_b - V_s]}_{} = 0$$

$$B Z_b i_b = B V_s$$


$$\text{Sub } I_b = B^T I_L$$

$$B Z_b B^T I_L = B V_s$$

$$Z = B Z_b B^T$$

$$+ \xleftarrow{V_k} -$$

(2)

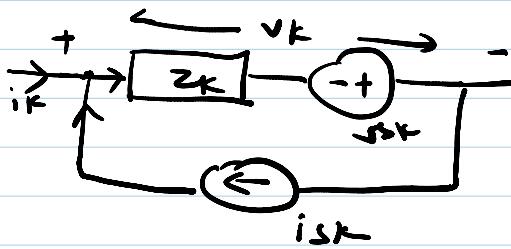

$$i_k = \frac{v_k + v_{sk}}{z_k} - i_{sk}$$

$$v_k = z_k i_k + z_k i_{sk} - v_{sk} \quad k = 1, 2, 3 \dots b$$

$$v_b = z_b I_b + z_b I_s - v_s$$

$$\beta v_b = 0 \quad KVL$$

$$\beta [z_b I_b + z_b I_s - v_s] = 0$$

$$\beta z_b I_b = \beta v_s - \beta z_b I_s$$


$$\boxed{\beta z_b \beta^T I_b = \beta v_s - \beta z_b I_s} \quad KVL$$

Generalised KVL equation in matrix form


III<sup>rd</sup>

$$\boxed{\mathbf{Y}_b \mathbf{Y}^T \mathbf{v}_t = \mathbf{I}_s - \mathbf{Y}_b \mathbf{v}_s} \quad KCL$$



\*

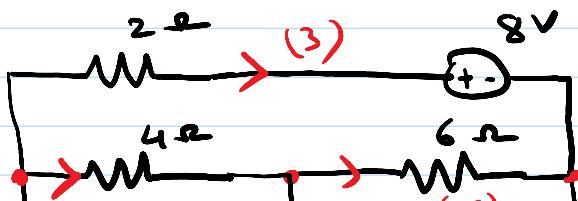

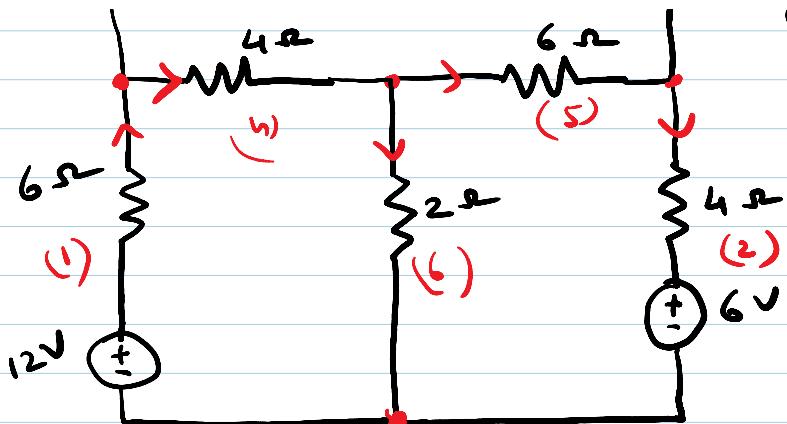Obtain N/W equilibrium eqn in matrix form



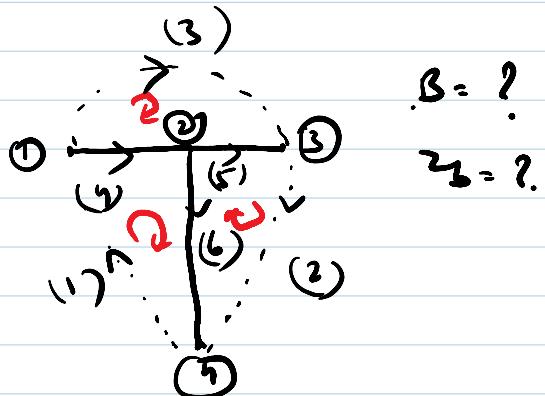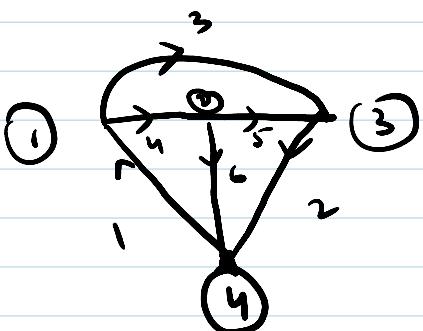to obtain N/W equilibrium  
eqn in matrix form  
using KVL.  
calculate loop currents



$$B = \begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 0 & 0 & 1 & 0 & 1 \\ 2 & 0 & 1 & 0 & 0 & 0 & 1 \\ 3 & 0 & 0 & 2 & 0 & 0 & 0 \\ 4 & 0 & 0 & 0 & 4 & 0 & 0 \\ 5 & 0 & 0 & 0 & 0 & 6 & 0 \\ 6 & 0 & 0 & 0 & 0 & 0 & 2 \end{matrix}$$

$$Z_b = \begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 6 & 0 & 0 & 0 & 0 & 0 \\ 2 & 0 & 4 & 0 & 0 & 0 & 0 \\ 3 & 0 & 0 & 2 & 0 & 0 & 0 \\ 4 & 0 & 0 & 0 & 4 & 0 & 0 \\ 5 & 0 & 0 & 0 & 0 & 6 & 0 \\ 6 & 0 & 0 & 0 & 0 & 0 & 2 \end{matrix}$$

KVL,  $B Z_b B^T I_L = B V_s - B Z_b I_s$   $I_s = 0$

$$\underline{\underline{B V_s}} = \underline{\underline{B Z_b B^T I_L}}$$

$$\begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix}_{3 \times 6} \begin{bmatrix} 12 \\ -6 \\ -8 \\ 0 \end{bmatrix} = \begin{bmatrix} 12 \\ -6 \\ -8 \end{bmatrix}$$

$$B \begin{bmatrix} 0 & 0 & 1 & -1 & 1 & 0 \end{bmatrix}_{3 \times 6} = \begin{bmatrix} -8 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$Bz_b = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & -1 & 0 \end{bmatrix} \begin{bmatrix} 6 \\ 4 \\ 2 \\ 4 \\ 6 \\ 2 \end{bmatrix}_{6 \times 1}$$

$$= \begin{bmatrix} 6 & 0 & 0 & 4 & 0 & 2 \\ 0 & 4 & 0 & 0 & 6 & -2 \\ 0 & 0 & 2 & -4 & -6 & 0 \end{bmatrix}$$

$$Bz_b \cdot B^T = \begin{bmatrix} 6 & 0 & 0 & 4 & 0 & 2 \\ 0 & 4 & 0 & 0 & 6 & -2 \\ 0 & 0 & 2 & -4 & -6 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & -1 \\ 0 & 1 & -1 \\ 1 & -1 & 0 \end{bmatrix}_{6 \times 6}$$

$$Bz_b B^T = \begin{bmatrix} 12 & -2 & -4 \\ -2 & 12 & -6 \\ -4 & -6 & 12 \end{bmatrix}$$

$$\begin{bmatrix} 12 \\ -6 \\ -8 \end{bmatrix} = \begin{bmatrix} 12 & -2 & -4 \\ -2 & 12 & -6 \\ -4 & -6 & 12 \end{bmatrix} \begin{bmatrix} I_{L_1} \\ I_{L_2} \\ I_{L_3} \end{bmatrix}$$

KVL


Solve this matrix

$$I_{L_1} = 0.55A$$

$$I_h = 0.55A$$

$$I_h = -0.866$$

$$I_{I_3} = -0.916A$$

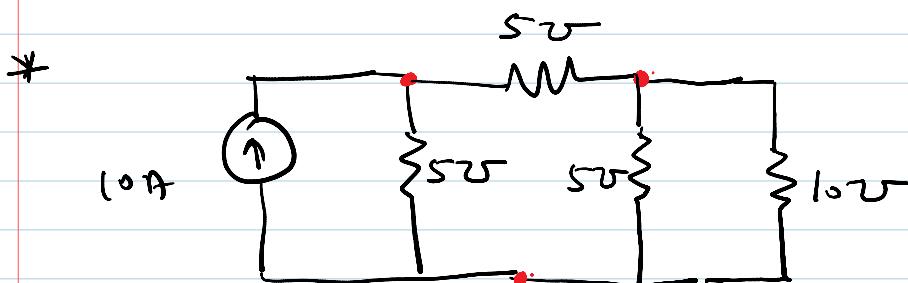

Obtain equilibrium  
eqn on node basis  
(KCL)

$$\Rightarrow \begin{array}{c} \text{Graph representation: } \\ \text{Nodes: } 1, 2, 3, 4 \\ \text{Branches: } (1,2), (1,3), (2,3), (2,4), (3,4) \\ \text{Boundary nodes: } 1, 4 \\ \text{Boundary edges: } (1,5), (4,6) \\ \text{Boundary currents: } I_b = ? \\ \text{Boundary voltages: } V_s = ? \end{array}$$

$$G = \frac{1}{3} \begin{bmatrix} 1 & 2 & 3 & 4 \\ 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix}$$

$$\stackrel{\text{KCL}}{=} \underbrace{G Y_b G^T}_{?} v_t = G I_b - G Y_b V_s \quad \boxed{V_s = 0}$$

$$G \cdot I_b = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -10 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$

$$G \cdot Y_b = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 5 & 0 & 0 & 0 \\ 0 & 5 & 0 & 0 \\ 0 & 0 & 5 & 0 \\ 0 & 0 & 0 & 10 \end{bmatrix}$$

$$= \begin{bmatrix} 5 & -5 & 0 & 0 \\ 0 & -5 & 5 & 10 \end{bmatrix}$$

$$Q^{-1}b \cdot Q^T = \begin{bmatrix} 5 & -5 & 0 & 0 \\ 0 & -5 & 5 & 10 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix}$$

$Q^{-1}b$        $Q^T$

$$= \begin{bmatrix} 10 & 5 \\ 5 & 20 \end{bmatrix}$$


KCL

$$\begin{bmatrix} 10 & 5 \\ 5 & 20 \end{bmatrix} \begin{bmatrix} vt_1 \\ vt_2 \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$


Solve  $vt_1$  &  $vt_2$

$$vt_1 = -8/7 v$$


$$vt_2 = 2/7 v$$

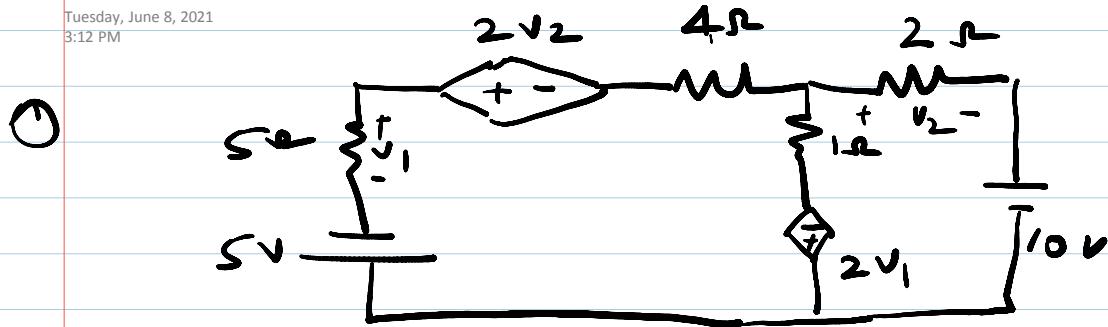


$I_1$  &  $I_2$ ?  
mesh

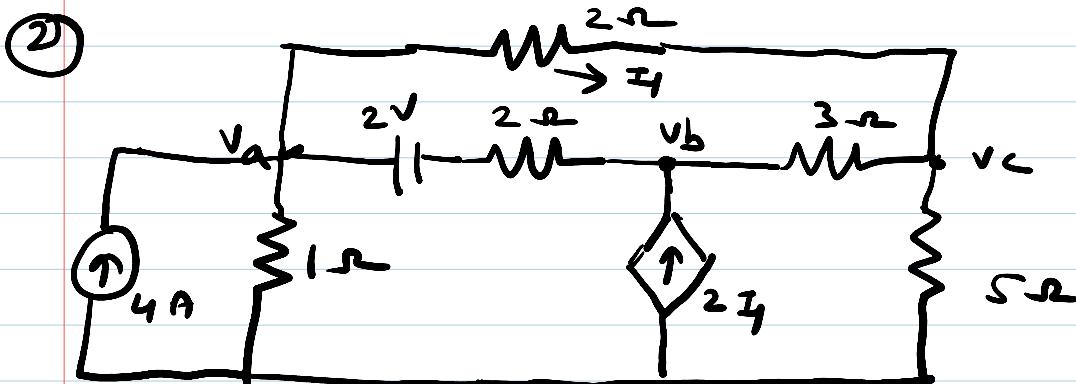

Node voltages  
 $v_a, v_b, v_c$ ?

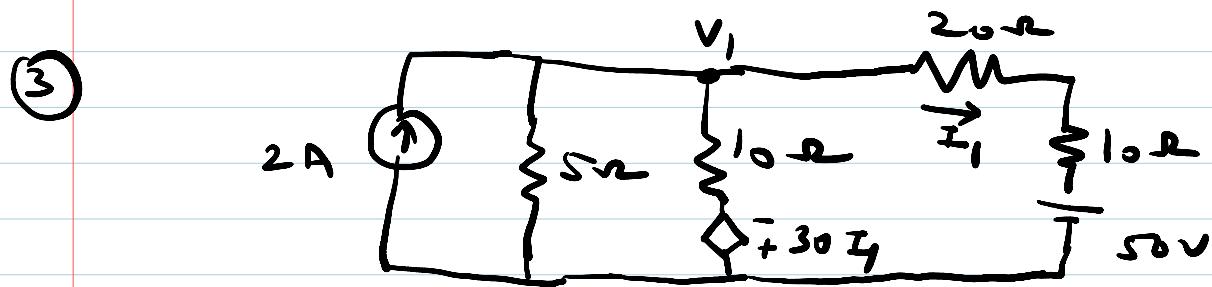

Find voltage across 5Ω?

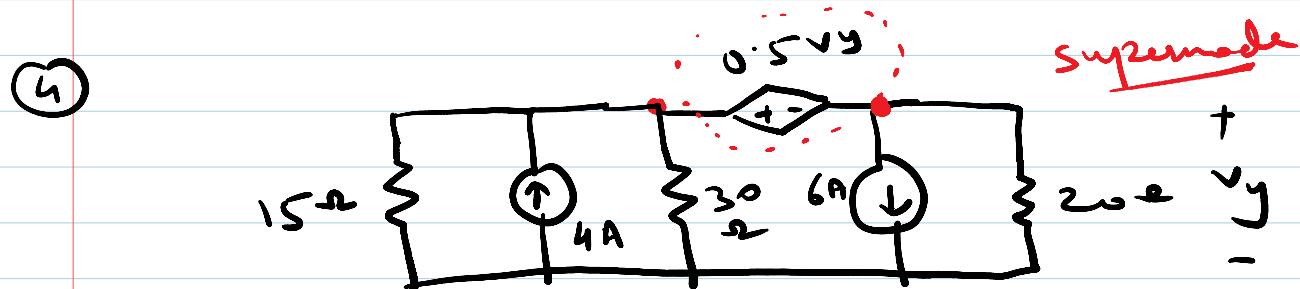

Supernode

Find  $v_y$ ?