
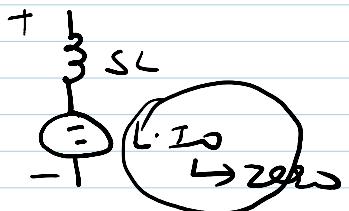


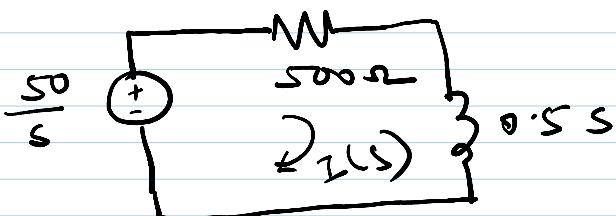In the given circuit, switch is closed at $t = 0$. There is no initial current through inductor. obtain $i(t)$ for $t > 0$ using L.T



KVL equation for mesh

$$\frac{50}{s} - 500I(s) - 0.5sI(s) = 0$$

$$\therefore \frac{50}{s} = I(s)[500 + 0.5s]$$

$$I(s) = \frac{50}{s(500 + 0.5s)}$$

$$\frac{50}{s(500 + 0.5s)} = \frac{A}{s} + \frac{B}{(0.5s + 500)} \Rightarrow P.F.E$$

$$A = \frac{50}{s(500 + 0.5s)} \Big|_{s=0} = \frac{50}{500} = 0.1$$

$$B = \frac{50}{s(500 + 0.5s)} \Big|_{s=-\frac{500}{0.5}} = -0.05$$


$$I(s) = \frac{0.1}{s} + \frac{-0.05}{(0.5s + 500)}$$

$$I(s) = \frac{0.1}{s} - \frac{0.1}{s + 1000}$$

$$i(t) = 0.1 - \frac{0.1}{1000} e^{-1000t} \text{ amp}$$

$$i(t) \rightarrow ILT = \boxed{\frac{s+1000}{0.1 u(t) - 0.1 e^{-1000t}}} \text{ amp}$$

(2)

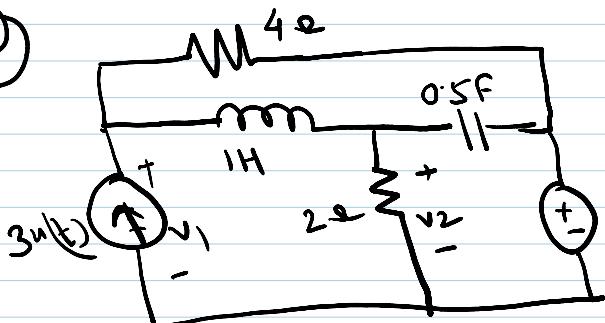

- no energy is stored initially


$$\textcircled{1} \quad v_1(s) \text{ & } v_2(s)$$

$$\textcircled{2} \quad v_1(t) \text{ & } v_2(t) \quad t > 0$$

$$\textcircled{3} \quad v_1(0), v_{1(\infty)}, v_2(0), v_{2(\infty)}$$

\textcircled{4} check the result in \textcircled{3} using initial value & final value theorem
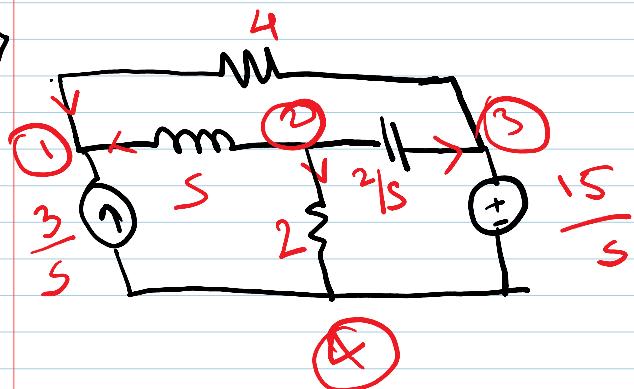
$$\hookrightarrow \frac{1}{Cs} = \frac{1}{0.5s} = \frac{2}{s}$$



$$v_3 = \frac{15}{s}$$

$$v_1(s) = v_1 \quad \& \quad v_2(s) = v_2$$

KCL at node \textcircled{1}

$$\frac{3}{s} + \frac{v_2(s) - v_1(s)}{s} + \frac{\frac{15}{s} - v_1(s)}{4} = 0$$

$$12 + 4v_2(s) - 4v_1(s) + 15 - 5v_1(s) = 0$$

$$(-4 - s)v_1(s) + 4v_2(s) + 27 = 0$$

$$(4 + s)v_1(s) - 4v_2(s) = 27 \quad \textcircled{1}$$

KCL at node \textcircled{2}

$$\frac{v_2(s)}{2} + \frac{v_2(s) - v_1(s)}{s} + \frac{v_2(s) - 15/s}{2/s} = 0$$

$$\frac{v_2(s)}{2} + \frac{v_2(s) - v_1(s)}{s} + \frac{sv_2(s) - 15}{2} = 0$$

$$sv_2(s) + 2v_2(s) - 2v_1(s) + 52v_2(s) - 15s = 0$$

$$v_2(s)[s + 2 + s^2] - 2v_1(s) - 15s = 0$$

* ... * .. * .. *

$$V_2 - V_L \rightarrow J = -15S - 15S$$

$$^*V_1(s) - ^*V_2(s)[s^2 + s + 2] = -15S \quad (2)$$

$$\begin{bmatrix} 4+s & -4 \\ 2 & s^2+s+2 \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} 27 \\ -15S \end{bmatrix}$$

$$\Delta =$$

$$V_1(s) = \frac{\Delta_1}{\Delta} \quad V_2(s) = \frac{\Delta_2}{\Delta}$$

$$V_1(s) = \frac{27s^2 + 87s + 54}{s(s+2)(s+3)}$$

$$V_2(s) = \frac{15s^2 + 6s + 54}{s(s+2)(s+3)}$$

(b) $V_1(t) \& V_2(t) = ?$

ILT \rightarrow P.F.E

$$V_1(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+3} \quad V_2(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+3}$$

$$A = 9$$

$$B = 6$$

$$C = 12$$

$$V_1(t) = 9u(t) + 6e^{-2t} + 12e^{-3t}$$

$$A = 9$$

$$B = 3$$

$$C = 3$$

$$V_2(t) = 9u(t) + 3e^{-2t} + 3e^{-3t}$$

(3) $t=0, V_1(0) = 9+6+12 = \underline{27v}$

$$t=\infty, V_1(\infty) = 9+0+0 = \underline{9wbs}$$

$$V_2(\infty) = 9+3+3 = \underline{15wbs}$$

$$V_2(\infty) = 9+0+0 = \underline{9wbs}$$

(4) Verify result of 3

$$\text{Initial value theorem } f(0^+) = \lim_{s \rightarrow \infty} [s f(s)] = 27$$

$$\text{Final value theorem } f(\infty) = \lim_{s \rightarrow 0} [s f(s)] = 9$$